

Current Electricity

Lesson 2: Equivalent Resistance

1. Equivalent Resistance in a circuit with Resistors connected in Series
2. Equivalent Resistance in a circuit with Resistors connected in Parallel
3. Equivalent Resistance in a circuit with Resistors connected both in Series and Parallel

YOUR TASKS: 6 Problems to be solved

Task 1: Follow Slides 2 to 4 and Solve Problem on Slide 5

Task 2: Follow Slides 6 and 7 and Solve Problem on Slide 8

Task 3: Follow Slides 9 and 11 and Solve Problem on Slide 12

Task 4: Follow Slide 13 and Solve Problem on Slide 14

Task 5: Follow Slide 15 and give solution for the Problem given on Slide 16 on Slide 17

Task 6: Follow Slide 18 and give solution for the Problem given on Slide 19 on Slide 20

Equivalent Resistance in a Circuit

When several resistors are connected in a circuit, the net or the total resistance of all the resistors in that circuit is called the Equivalent Resistance.

In Circuit, if you see a component, with the following design, then it is a resistor





Ohm, is the unit of resistance; ohm has the following symbol

Ω

In Circuit, a battery or a power source is represented by the design on the right.

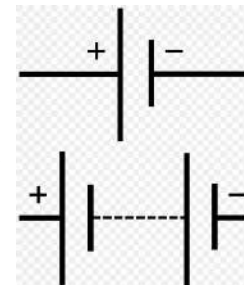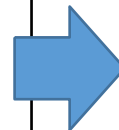
The top is for a single battery; the bottom is for two batteries.



Resistors Connected in Series in a Circuit:

GUIDED PRACTICE 1

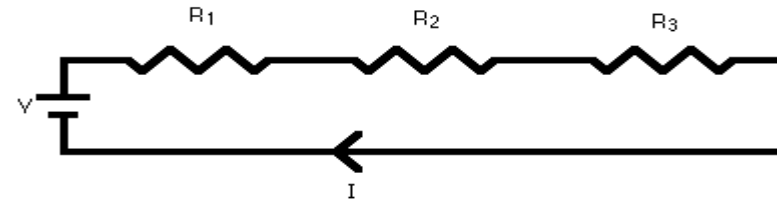Series means one after the other in the same row. An example of a circuit with three resistors connected in a series is shown below:



The Equivalent Resistance of a circuit with multiple resistors in series is the sum of resistance values of the connected resistors.

For the above circuit, the Equivalent Resistance is given by:

$$R_{\text{series}} = R_1 + R_2 + R_3$$

Let us assign values for R_1 R_2 R_3

$$R_1 = 5 \text{ ohm}$$

$$R_2 = 8 \text{ ohm}$$

$$R_3 = 12 \text{ ohm}$$

The equivalent resistance of this circuit is:

$$R_{\text{series}} = R_1 + R_2 + R_3$$

$$R_{\text{series}} = 5 + 8 + 12 = 25 \text{ ohm}$$

Resistors Connected in Series in a Circuit: Guided Practice 1

A circuit has four resistors connected in a series with resistances of 0.5 ohm, 300 mohm (milliohm), 60,000 μ ohm (microohm), and 75cohm (centiohm); find the equivalent resistance of the circuit.

Solution

Process: Convert all resistance values into ohms (use metric ladder) and then add them up

$$R_{\text{series}} = R_1 + R_2 + R_3 + R_4$$

$$R_1 = 0.5 \text{ ohm}$$

$$R_2 = 300/1000 = 0.3 \text{ ohm}$$

$$R_3 = 60,000/1000000 = 0.06 \text{ ohm}$$

$$R_4 = 75/100 = 0.75 \text{ ohm}$$

$$R_{\text{series}} = R_1 + R_2 + R_3 + R_4$$

$$= 0.5 + 0.3 + 0.06 + 0.75 = 1.61 \text{ ohm}$$

**METRIC LADDER is
on my Website
under the Task for
April 20, 2020**

Resistors Connected in Series in a Circuit: Independent Practice 1

A circuit has four resistors connected in a series with resistances of 0.35 ohm, 0.3 centiohm (centiohm), 48,200 μ ohm (microohm), and 75 daohm (decaohm); find the equivalent resistance of the circuit.


Solution

**METRIC LADDER is
on my Website
under the Task for
April 20, 2020**

TWO Resistors Connected in Parallel in a Circuit

GUIDED PRACTICE – INVERSING THE SUM OF RATIOS METHOD

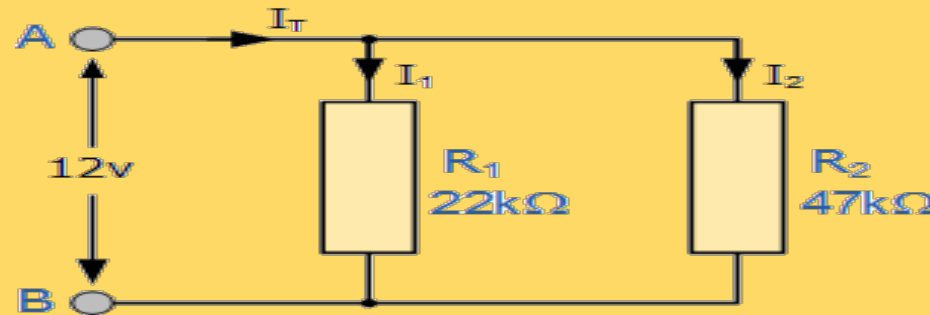Parallel means side by side as separate rows. An example of a circuit with two resistors connected in parallel is given is shown below: Ω is the symbol for ohm.



The Equivalent Resistance of a circuit with two resistors in parallel is given by

For the above circuit, the Equivalent Resistance is given by:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Let us assign values for R_1 and R_2

$R_1 = 5 \text{ ohm}$

$R_2 = 8 \text{ ohm}$



The equivalent resistance of this circuit is:

$$1/R_{EqParallel} = 1/R_1 + 1/R_2$$

$$1/R_{EqParallel} = 1/5 + 1/8$$

$$1/R_{EqParallel} = 0.2 + 0.125 = 0.325 \text{ ohm}$$

$R_{EqParallel}$ is the inverse of $1/R_{EqParallel}$

$$\text{Therefore, } R_{EqParallel} = 1/0.325 = 3.07 \text{ ohm}$$

TWO Resistors Connected in Parallel in a Circuit

GUIDED PRACTICE: PRODUCT BY SUM METHOD

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

Putting the right-hand side over the same common denominator,

$$\frac{1}{R} = \frac{R_2 + R_1}{R_1 R_2}$$

Inverting both sides,

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

Hence, for *two* resistors in parallel,

$$\text{combined resistance} = \frac{\text{product of resistances}}{\text{sum of resistances}}$$

It is useful to learn this formula by heart.

Let us solve the same Problem in Slide 6 by the Product Over Sum Method

$$\begin{aligned} R_{\text{EqParallel}} &= (5 \times 8)/(5+8) \\ &= 40/13 \\ &= 3.07 \end{aligned}$$

You get the same answer in both the methods. So, you may choose to solve problems of two resistors in parallel by any one of the two methods

TWO Resistors Connected in Parallel in a Circuit


INDEPENDENT PRACTICE: PRODUCT BY SUM METHOD

Two resistors of resistance values of 15 ohm and 25 ohm are connected in parallel in a circuit – find the equivalent resistance of the circuit – **you can solve by any one of the two methods shown in slides 6 and 7**

TWO Resistors Connected in Parallel in a Circuit

GUIDED PRACTICE: PRODUCT BY SUM METHOD

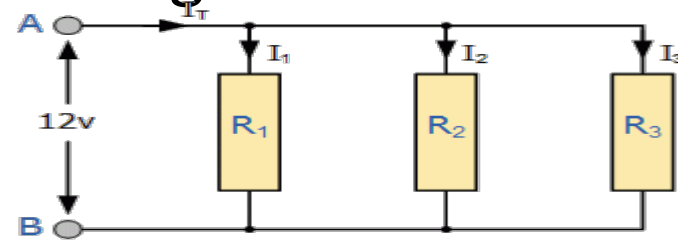Parallel means side by side as separate rows. An example of a circuit with three resistors connected in parallel is given is shown below:



The Equivalent Resistance of a circuit with multiple resistors in parallel is given by

For the above circuit, the Equivalent Resistance is given $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

Let us assign values for R_1 R_2

$$R_1 = 5 \text{ ohm}$$

$$R_2 = 8 \text{ ohm}$$

$$R_3 = 12 \text{ ohm}$$

The equivalent resistance of this circuit is:

$$1/R_{\text{Parallel}} = 1/R_1 + 1/R_2 + 1/R_3$$

$$1/R_{\text{Parallel}} = 1/5 + 1/8 + 1/12$$

$$1/R_{\text{Parallel}} = 0.2 + 0.125 + 0.083 = 0.408 \text{ ohm}$$

R_{parallel} is the inverse of $1/R_{\text{Parallel}}$

$$\text{Therefore, } R_{\text{parallel}} = 1/0.408 = 2.451 \text{ ohm} = 2.5 \text{ ohm}$$

NOTE: PRODUCT BY SUM METHOD
GETS COMPEX IF YOU HAVE MORE
THAN TWO RESISTORS IN A
CIRCUIT.

THIS IS SHOWN IN NEXT SLIDE

THREE Resistors Connected in Parallel in a Circuit

GUIDED PRACTICE: PRODUCT BY SUM METHOD

In the Product by Sum Method for THREE Resistors,

Can be simplified $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

$$R_{eq} = (R_1 * R_2 * R_3) / (R_2 * R_3) + (R_1 * R_3) + (R_1 * R_2)$$

You get the same answer in both the methods. So, you may choose to solve problems of two resistors in parallel by any one of the two methods

Let us now work with the values of resistance given in slide 9 for R_1 R_2 R_3

$$R_1 = 5 \text{ ohm}$$

$$R_2 = 8 \text{ ohm}$$

$$R_3 = 12 \text{ ohm}$$



$$\begin{aligned} R_{eq} &= (R_1 * R_2 * R_3) / (R_2 * R_3) + (R_1 * R_3) + (R_1 * R_2) \\ &= (5 \times 8 \times 12) / (8 \times 12) + (5 \times 12) + (5 \times 8) \\ &= 480 / (96 + 60 + 40) \\ &= 480 / 196 \\ &= 2.449 = 2.5 \text{ ohm} \end{aligned}$$

THREE Resistors Connected in Parallel in a Circuit


INDEPENDENT PRACTICE: PRODUCT BY SUM METHOD

Three resistors of resistance values of 8.5 ohm, 12.3 ohm and 2.5 ohm are connected in parallel in a circuit – find the equivalent resistance of the circuit – **you can solve by any one of the two methods shown in slides 9 or 11**

Resistors Connected in Series and Parallel in a Circuit

Guided Practice - 1

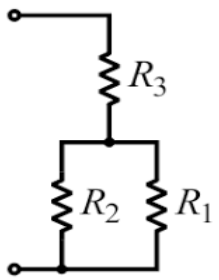An example of a circuit with resistors connected in series and parallel is shown below:



In this circuit, R_1 and R_2 are in parallel and R_3 is in series with the combo set of R_1 and R_2
So, find the equivalent resistance of R_1 and R_2 and then add it to R_3

Let us assign values for R_1 R_2 R_3

$$R_1 = 5 \text{ ohm}$$

$$R_2 = 8 \text{ ohm}$$


$$R_3 = 12 \text{ ohm}$$

Step 1: Equivalent resistance of R_1 and R_2 by Product Over Sum Method:
 $= (5 \times 8) / (5 + 8) = 40 / 13 = 3.08 \text{ ohm}$
Step 2: Add Answer from Step 1 to R_3
 $= 3.08 + 12 = 15.08 \text{ ohm}$

Solution: The Equivalent Resistance of the Given Circuit = 15.08 ohm

Resistors Connected in Series and Parallel in a Circuit

Independent Practice - 1

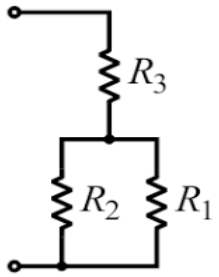

Let us assign values for R_1 R_2 R_3

$$R_1 = 15 \text{ ohm}$$

$$R_2 = 3 \text{ ohm}$$

$$R_3 = 1 \text{ ohm}$$

Step 1: Equivalent resistance of R_1 and R_2 by Product Over Sum Method:

$$= \quad \quad \quad \text{ohm}$$

Step 2: Add Answer from Step 1 to R_3

$$= \quad \quad \quad \text{ohm}$$


Solution: The Equivalent Resistance of the Given Circuit = ohm

Resistors Connected in Series and Parallel in a Circuit

Guided Practice -2

Determine the Equivalent Resistance of the following circuit; Show complete work.
Note: Ω is the symbol for ohm.

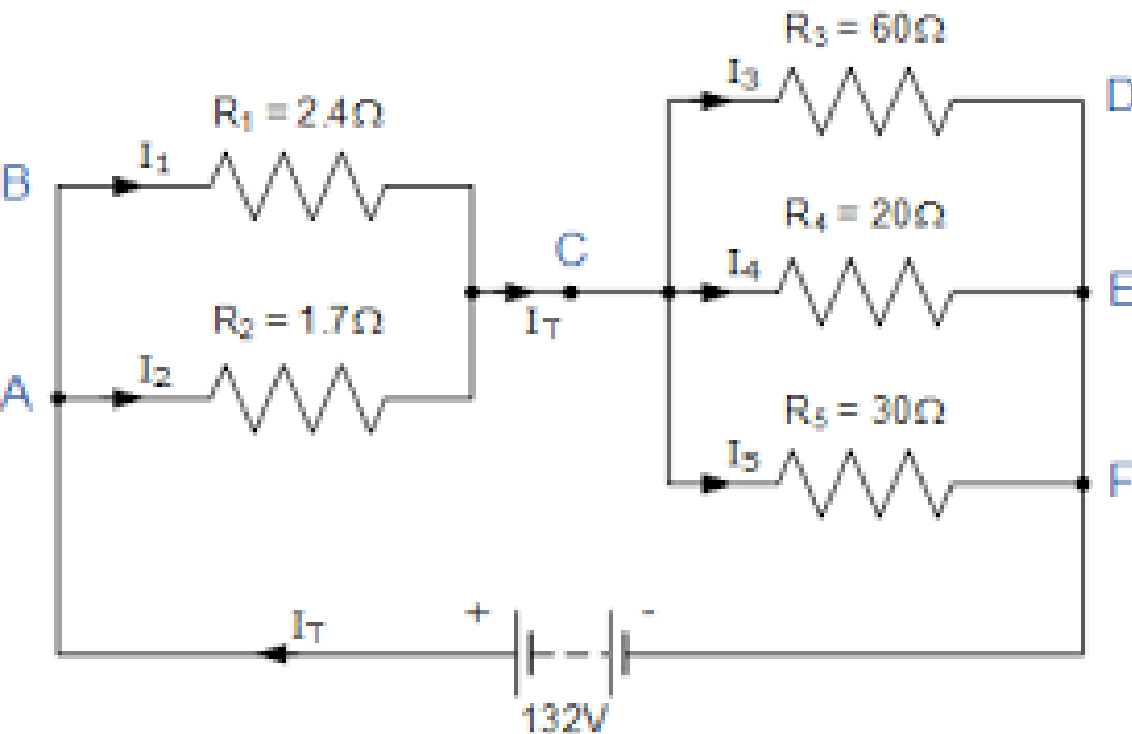Two sets of Parallely connected resistors are connected in series: Find the Equivalent Resistance of the set R_1 and R_2 and then find the Equivalent Resistance of the set R_3 , R_4 and R_5 - Finally add both the Equivalent Resistances.



Step 1: Equivalent Resistance of the set R_1 and R_2 by Product by Sum Method

$$= (2.4 \times 1.7) / (2.4 + 1.7) = 4.08 / 4.1 = 0.995 \text{ ohm}$$

Step 2: Equivalent Resistance of the set R_3 , R_4 and R_5 by Product by Sum Method

$$= (60 \times 20 \times 30) / [(20 \times 30) + (60 \times 30) + (60 \times 20)] = 36,000 / 3,600 = 10 \text{ ohm}$$


Step 3: Sum of Answers of Step 1 and Step 2

$$= 0.995 + 10 = 10.995 \text{ ohm}$$

Resistors Connected in Series and Parallel in a Circuit

Independent Practice -2

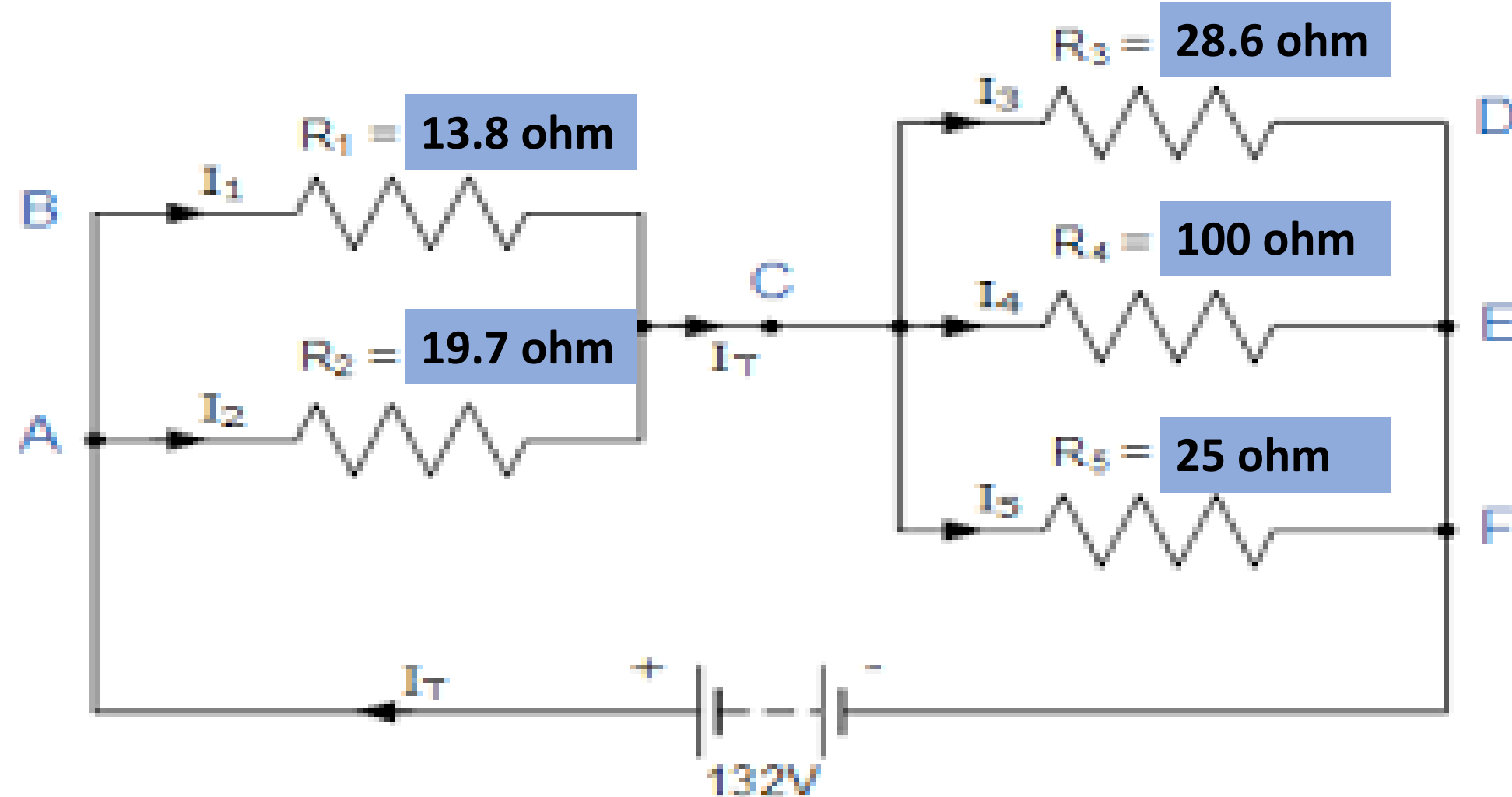Determine the Equivalent Resistance of the following circuit; Show complete work



Show
work
on next
slide

Your complete work for Problem on Slide 11

Step 1: Equivalent Resistance of the set R_1 and R_2 by Product by Sum Method

$$= \text{ohm}$$

Step 2: Equivalent Resistance of the set R_3 , R_4 and R_5 by Product by Sum Method

$$= \text{ohm}$$

Step 3: Sum of Answers of Step 1 and Step 2


$$= + = \text{ohm}$$

Resistors Connected in Series and Parallel in a Circuit

Guided Practice -3

Determine the Equivalent Resistance of the following circuit; Show complete work. Clue: Two sets of Parallely connected resistors are connected in series with three resistors already connected in series:

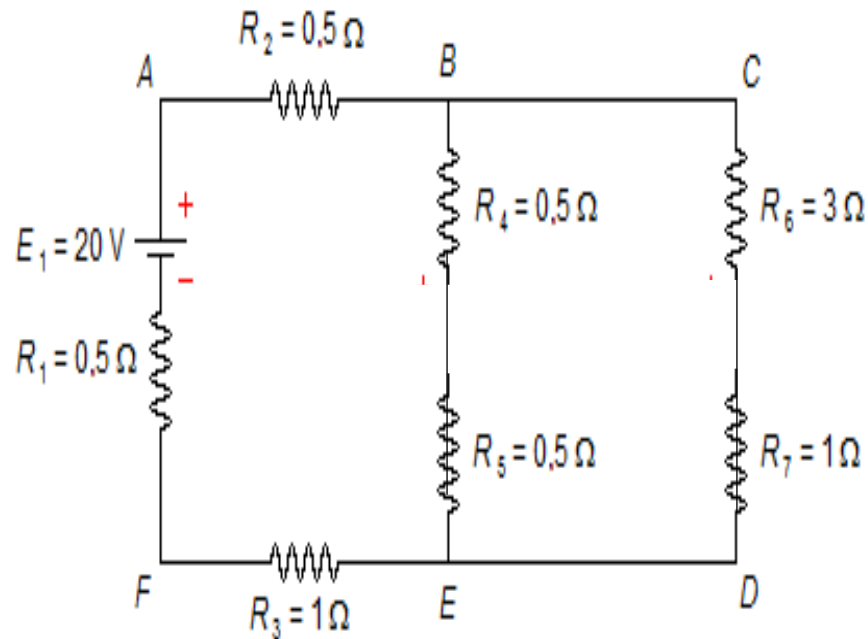First find the resistance of set R_4 and R_5 ; next, find the resistance of R_6 and R_7 . Then, find the Equivalent Resistance of the parallel connection between the set R_4 and R_5 and the set R_6 and R_7 - Finally add the Equivalent Resistance to the sum of $R_1 + R_2 + R_3$



Step 1: Resistance of the series set R_4 and R_5

$$= (0.5 + 0.5) = 1\ \text{ohm}$$

Step 2: Resistance of the series set R_6 and R_7

$$= (3 + 1) = 4\ \text{ohm}$$

Step 3: Equivalent Resistance of the two sets from Step 1, and Step 2 by Product by Sum Method

$$= (1 \times 4) / (1 + 4) = 4/5 = 0.8\ \text{ohm}$$


Step 4: Total Series Resistance of the Circuit: Add answer from Step 3 to $R_1 + R_2 + R_3$

$$= 0.8 + 0.5 + 0.5 + 1 = 2.8\ \text{ohm}$$

Resistors Connected in Series and Parallel in a Circuit

Independent Practice -3 – SHOW WORK ON NEXT SLIDE

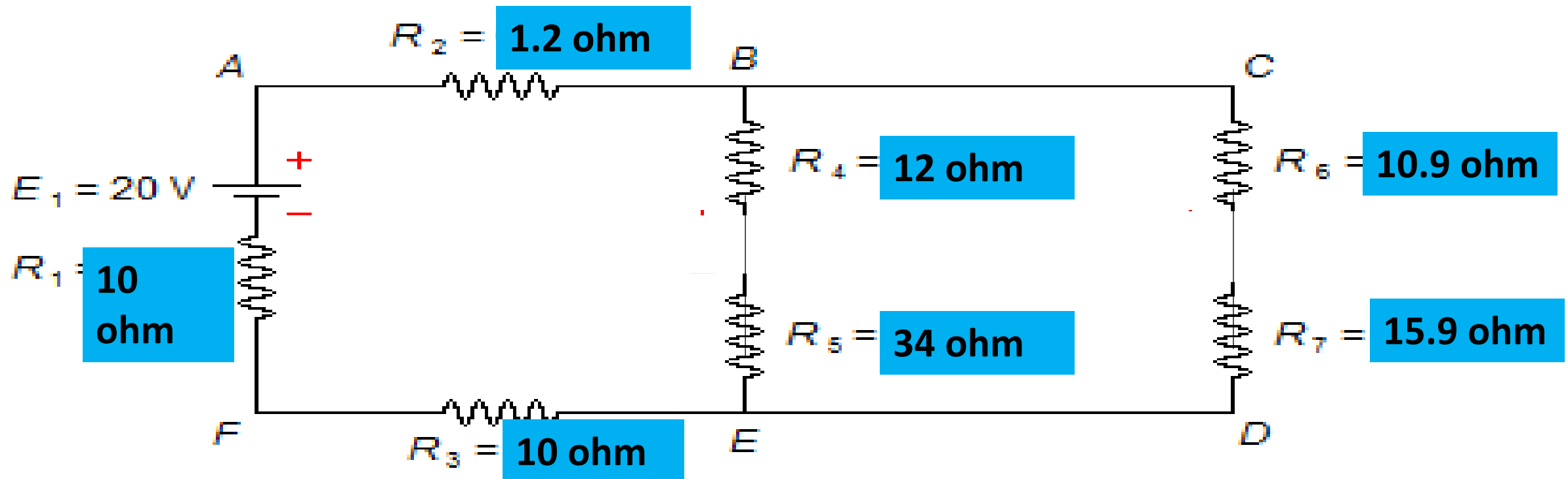Follow Slide 20, and determine the Equivalent Resistance of the following circuit;
Show complete work on next slide.



Resistors Connected in Series and Parallel in a Circuit

Guided Practice -3

Follow Slide 19 and show your complete work for the solution for the Problem on Slide 20

Step 1: Resistance of the series set R_4 and R_5
= ohm

Step 2: Resistance of the series set R_6 and R_7
= ohm

Step 3: Equivalent Resistance of the two sets from Step 1, and Step 1 by Product by Sum Method
= ohm

Step 4: : Total Series Resistance of the Circuit: Add answer from Step 3 to $R_1 + R_2 + R_3$
= = 2.8 ohm