

# Electricity and Circuits

# Electric Charges

- Three particles that make up an atom:

–Protons


–Neutrons

–Electrons

POSITIVE

NEUTRAL

NEGATIVE

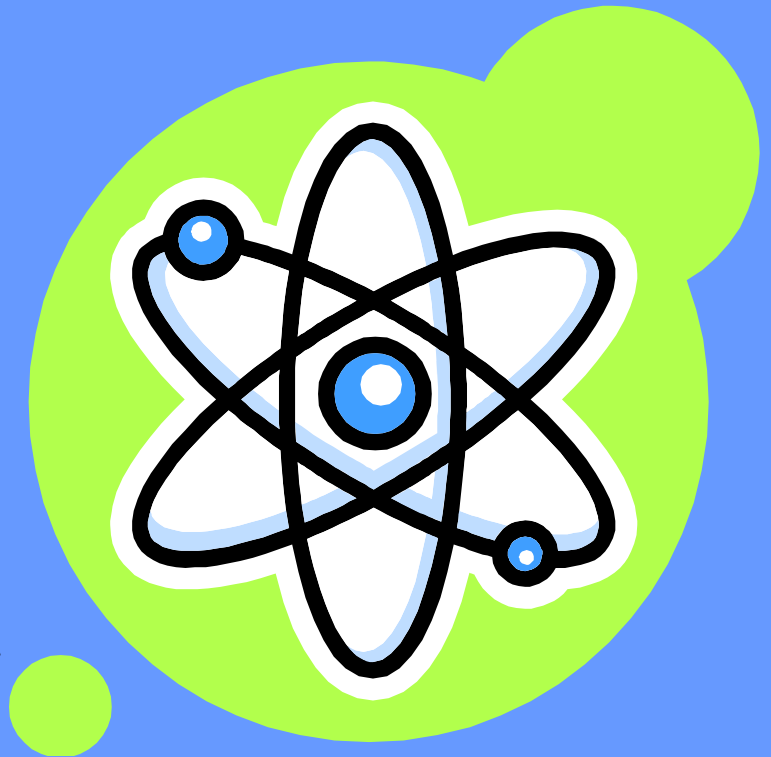


# The Flow of Charges

- Which subatomic particle can move from one object to another?
  - Electrons!
- What does the addition of electrons do to the charge of an object?
  - The object will become **NEGATIVELY** charged.
- What does the removal of electrons do to the charge of an object?
  - The object will become **POSITIVELY** charged.




# How Charges Interact

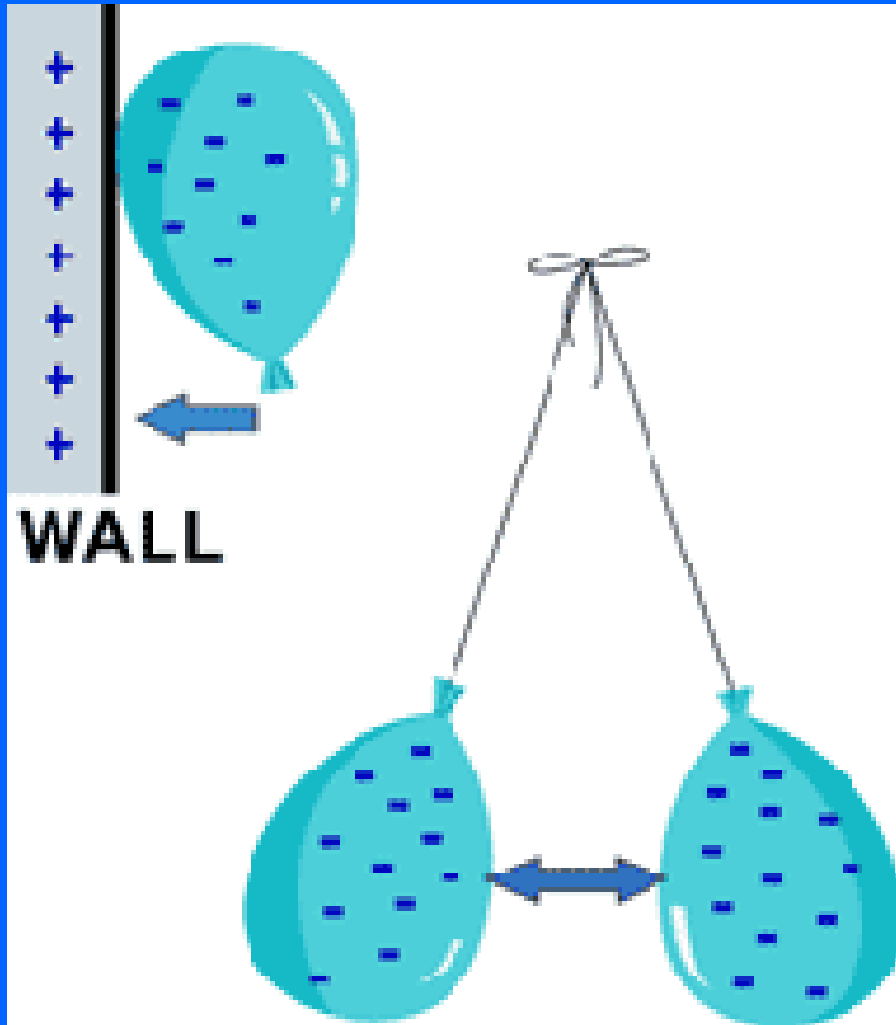

- When two objects with the SAME charge come into contact, they repel.
- When two objects with DIFFERENT charges come into contact, they attract.
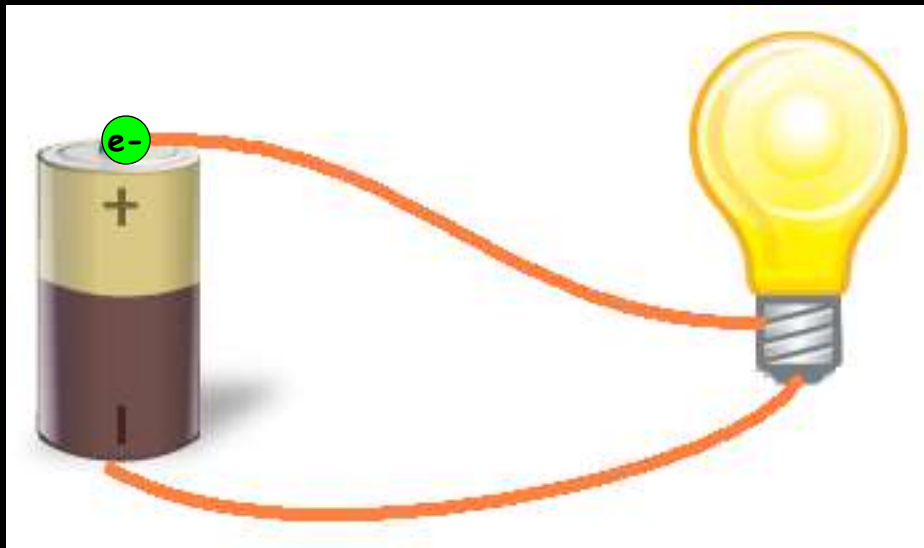
# Electric Current

- What is an electric current?
  - The continuous flow of electric charges through a material.
- What is the unit of measurement for current?
  - amperes (A) or amps: the amount of charge flowing past a point in a certain amount of time.



# Potential Difference


- What's potential energy (PE)?
- On a roller coaster, where does the car have more potential energy?
- Can the car move from an area of low PE to high PE without the help of a motor?

- **It's the same for electric current!**
  - The **charges in a current** are like the **roller coaster cars**.
  - The **track** is like the **wires**.
  - The **motor** that gets the cars to the top of the first hill is like the **battery**.



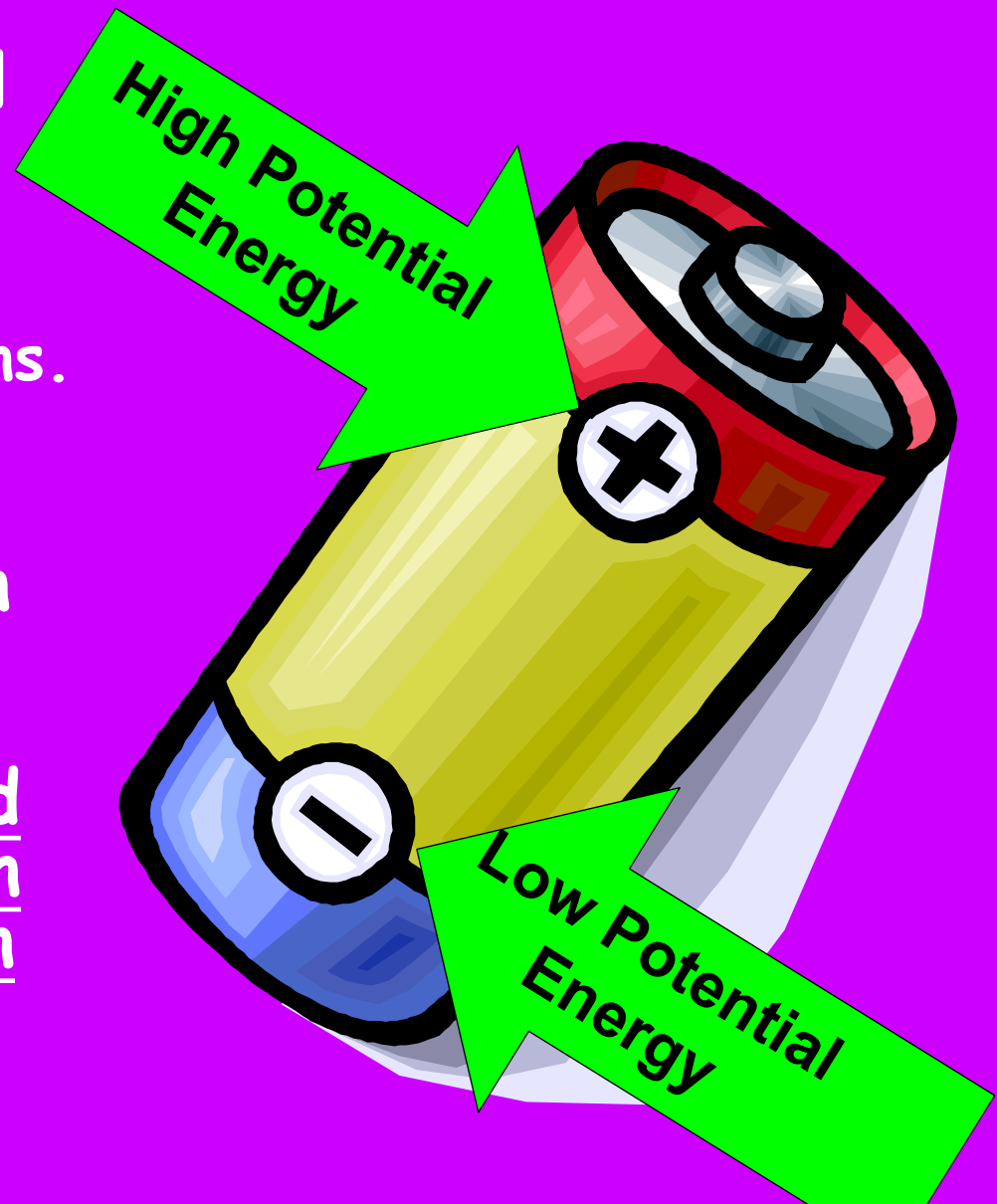
# Potential Difference Cont.

- So what is Potential Difference?
  - The difference in potential energy between two locations.
- The difference between a rollercoaster and an electric current is that the potential difference is caused by the difference in electrical charges in two locations, not height.


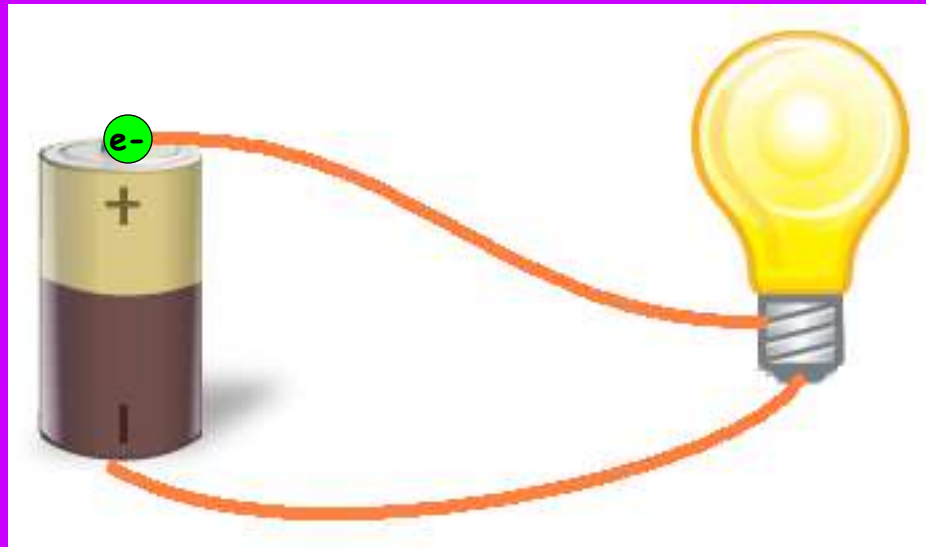
# Potential Difference Cont.

- Electric charges will always flow from a region of high potential energy to a region of low potential energy.
- When the charge reaches the positive terminal and enters the battery, it gains electric potential energy as it travels through the battery to the negative terminal.





# Voltage



- What is it?
  - Another term for potential difference.
- What unit is used to measure voltage?
  - Volts (V)
- So in a 9-volt battery, when an electric charge moves from the negative terminal, through the battery, to the positive terminal, how much potential energy does the charge gain?
  - 9 volts!

# Basic Circuits


- A circuit is a path through which electricity can flow.
- Most circuits have three parts: a source of electrical energy, a load, and wires that connect the two.

**Create a basic circuit. Use only a battery, two wires, and a bulb. Draw your circuit on your notes page.**


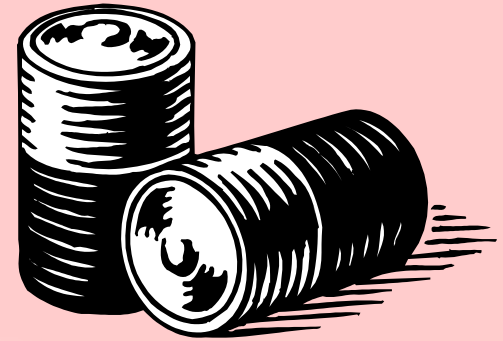
# Parts of a Circuit

- Energy Source - A circuit needs an energy source to push a charge through the circuit.
  - Examples?
- Load - a load is a device in a circuit that operates using electrical energy.
  - Examples?
- Conductor - a conductor is a material that allows electrical energy to flow through it easily.
  - What makes a good conductor?
  - Examples?




# Parts of a Circuit Cont.

- Resistor - a resistor is an object added to a circuit that restricts the flow of electrical energy.
  - Resistors inhibit the flow of electric current by producing a voltage drop when current passes through them. They limit current and cause some electric energy to be given off as heat.
  - Examples?
- Switch - a switch is a device that is used to control the flow of current through a circuit.
  - A switch works by separating (open) or bringing together (closed) two conductors attached to a circuit.




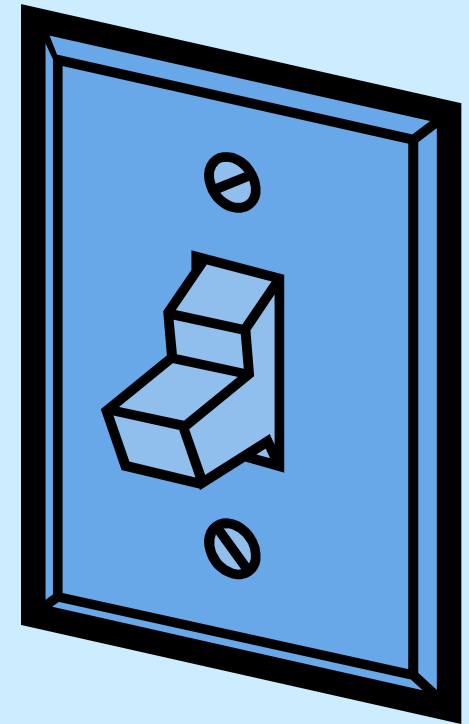
# Circuit Switches

- Add a switch to your circuit. See what happens when you open and close the switch.
- On your notes, draw a circuit with an open switch and a closed switch. Indicate whether the light is on or off.
- When an electric current reaches an open switch, the current stops.
  - This creates an open circuit.
- When an electric current reaches a closed switch, the current continues.
  - This creates a closed circuit.
- Why would you want a switch in a circuit?



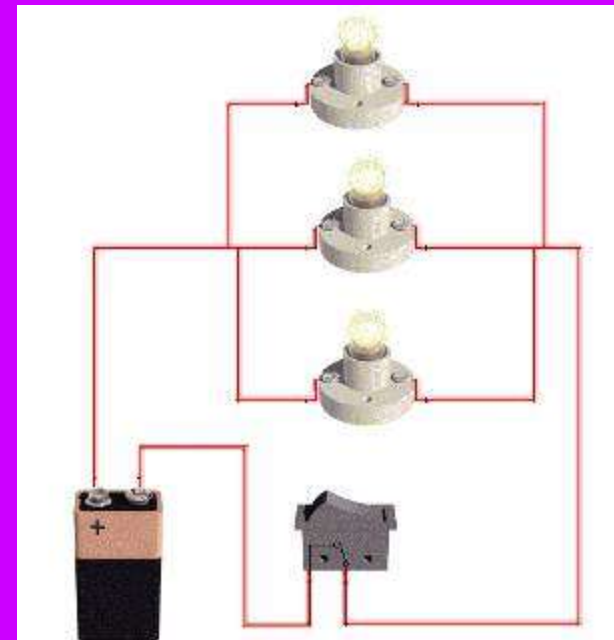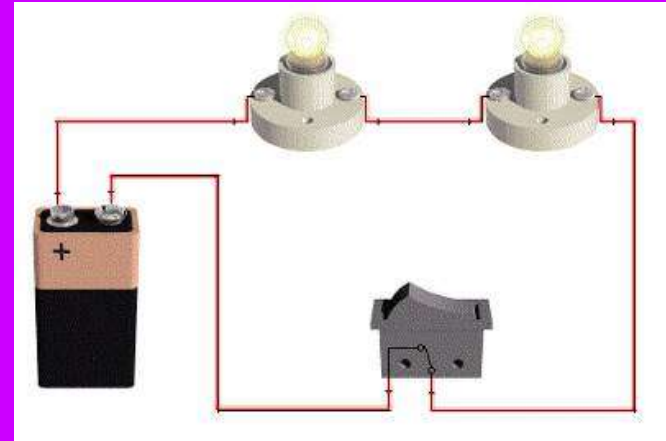
# Types of Circuits

- Two types of circuits:
  - Series Circuit
    - Provides only one possible path for the flow of current.
  - Parallel Circuit
    - Offers more than one path for the flow of electricity.




# Series Circuits

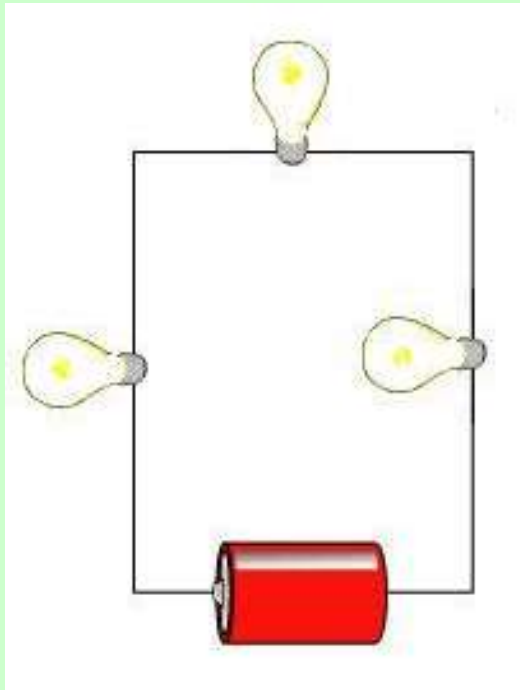

- In a series circuit, the loads are set up in a series, or line, that requires the current to flow through one load before passing through the next.
- Draw your circuit on your notes sheet.
- Use arrows to indicate the direction the electric current is traveling.

# Parallel Circuits

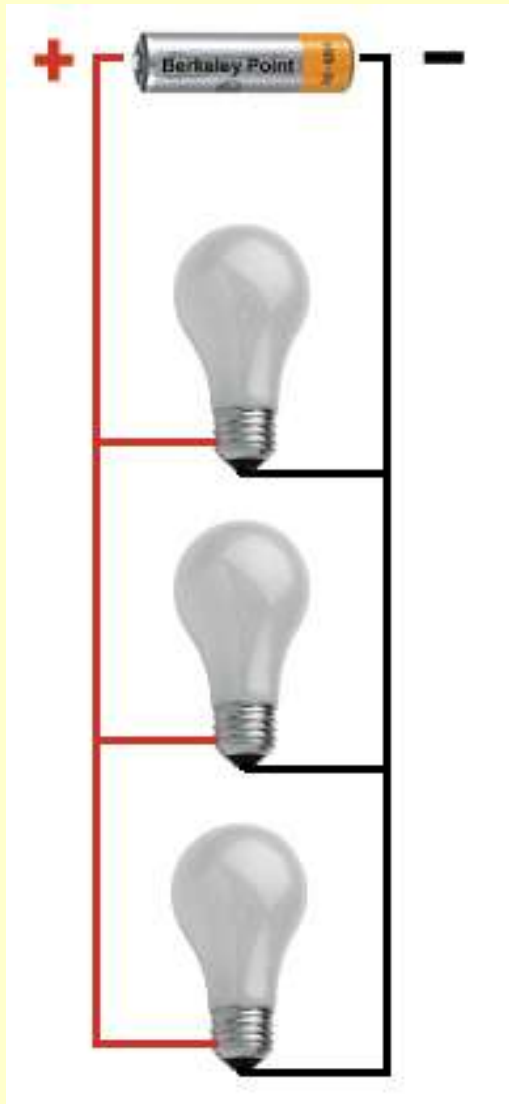

- In a parallel circuit, each load has its own path for electricity.
- Draw your circuit on your notes sheet.
- Use arrows to indicate the directions the electric current is traveling.