

Introduction to **ELECTRICAL CIRCUIT DIAGRAMS**




SciencePoint

A SIMPLE ELECTRICAL CIRCUIT

Teacher Guide

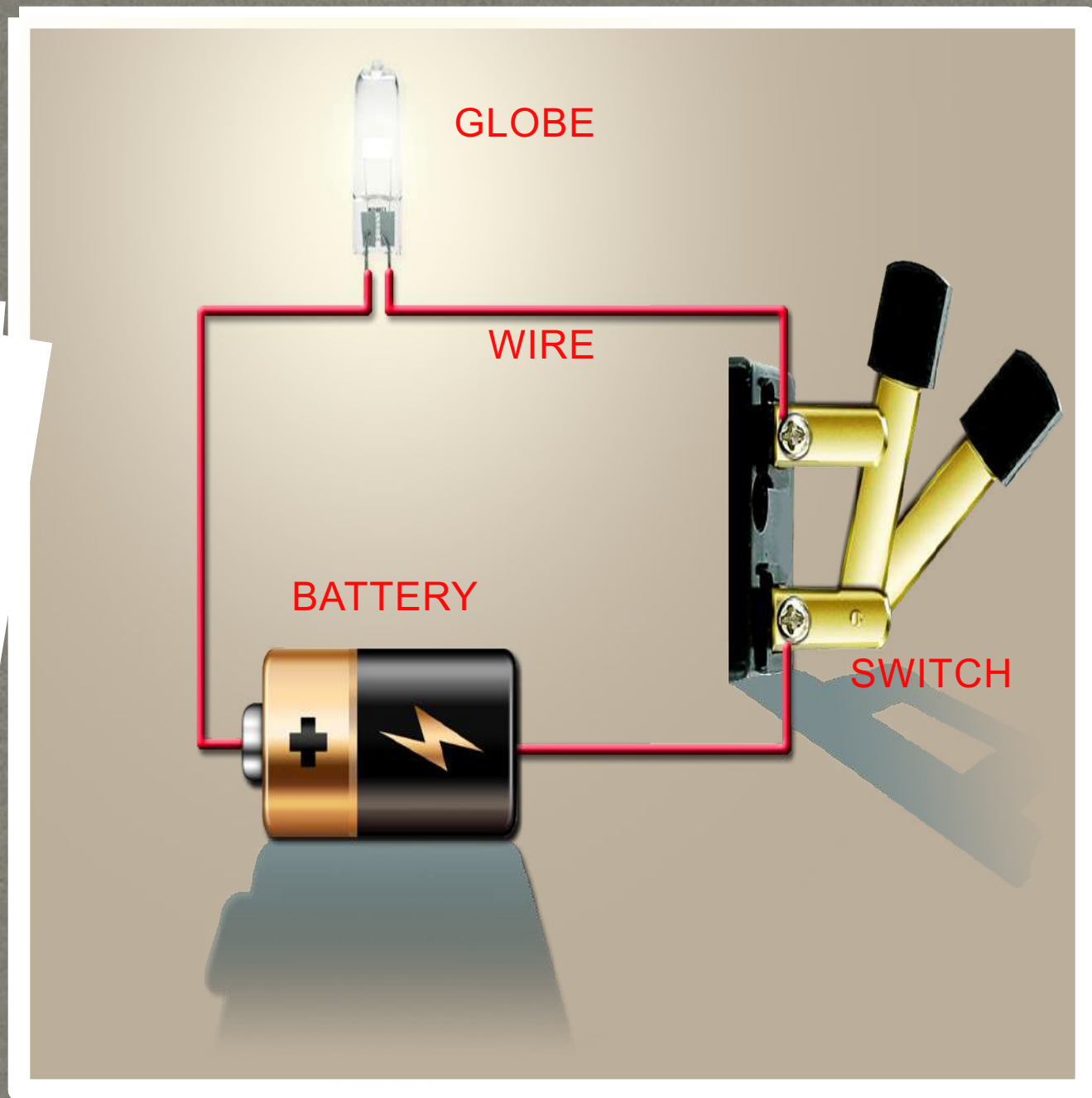
Click on the light switch to turn the globe on and off.



A SIMPLE ELECTRICAL CIRCUIT

Teacher Guide

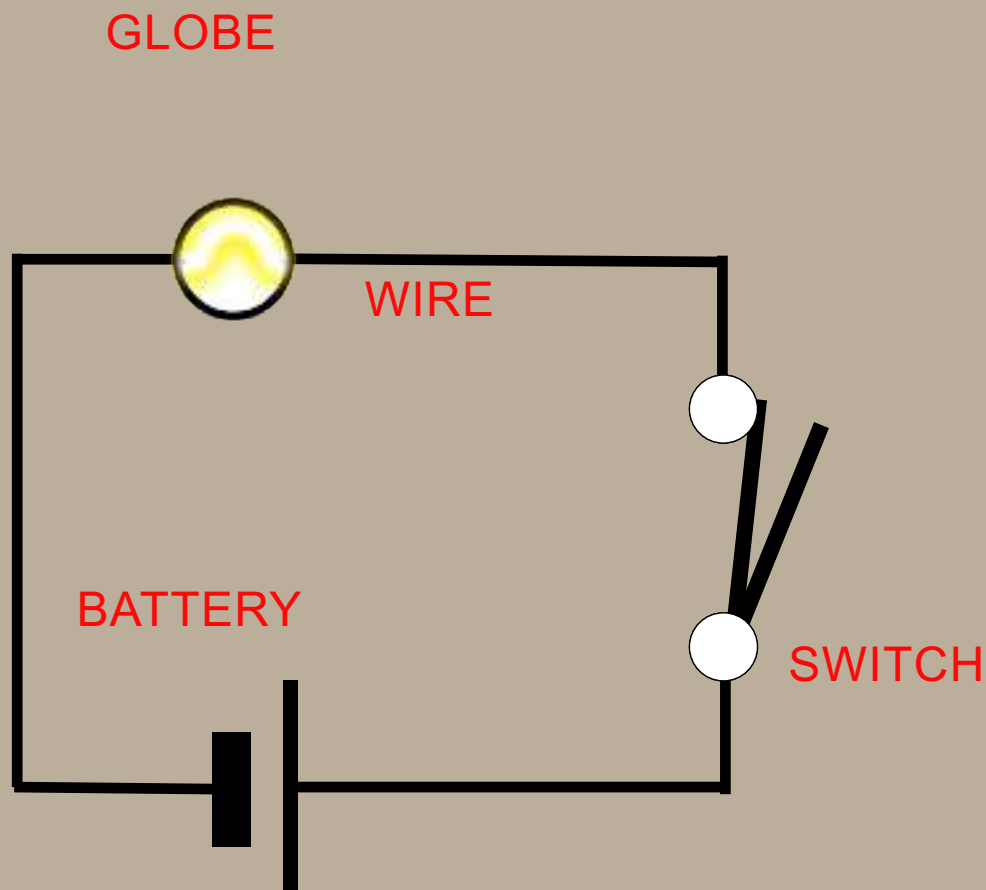
Click on the round white terminals of the switch or the black bar of the switch to light switch to turn the globe on and off.




COMMON ELECTRICAL SYMBOLS

Teacher Guide


Click to display each component.

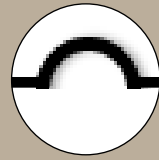


GLOBE

 

BATTERY
x1

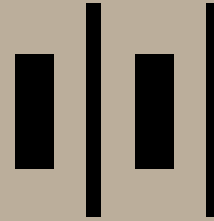

BATTERIES
x2

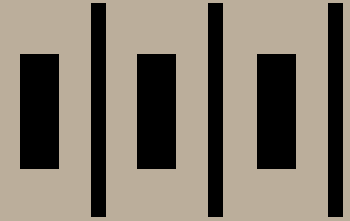

BATTERIES
x3




SWITCH
CLOSED
(ON)



SWITCH
OPEN
(OFF)



WIRE

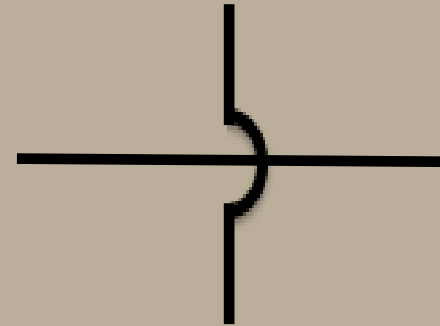


WIRES CROSSING
BUT NOT CONNECTED


COMMON ELECTRICAL SYMBOLS

Teacher Guide

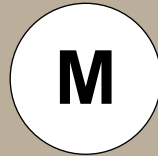
This is a static slide.
There are no animations.




ELECTRIC
MOTOR

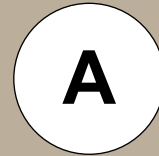

AMMETER

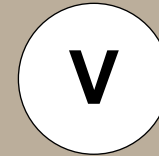

VOLTMETER

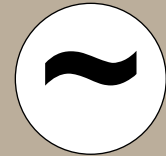


AC
VOLTAGE
SOURCE




FUSE



RESISTOR

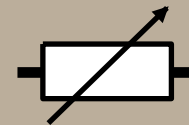

VARIABLE
RESISTOR

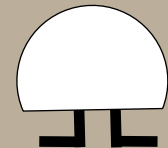


ELECTRIC
BELL

ELECTRICAL CIRCUITS SERIES

Teacher Guide

Click on the light switch to turn the globe on and off.

Click on page to display text.

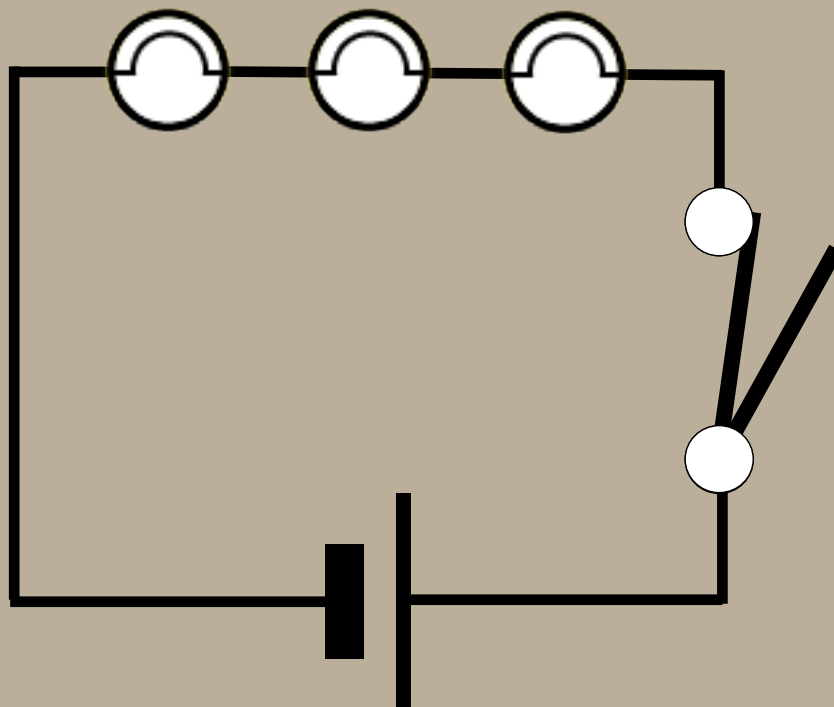

DIFFERENCES BETWEEN SERIES & PARALLEL CIRCUITS

Teacher Guide



Click on the light switches to turn the globes on and off.

Note the relative brightness of globes.

Click on an **illuminated** globe to "break" it. Note the effect.

Click red arrow to reset (repair globes).

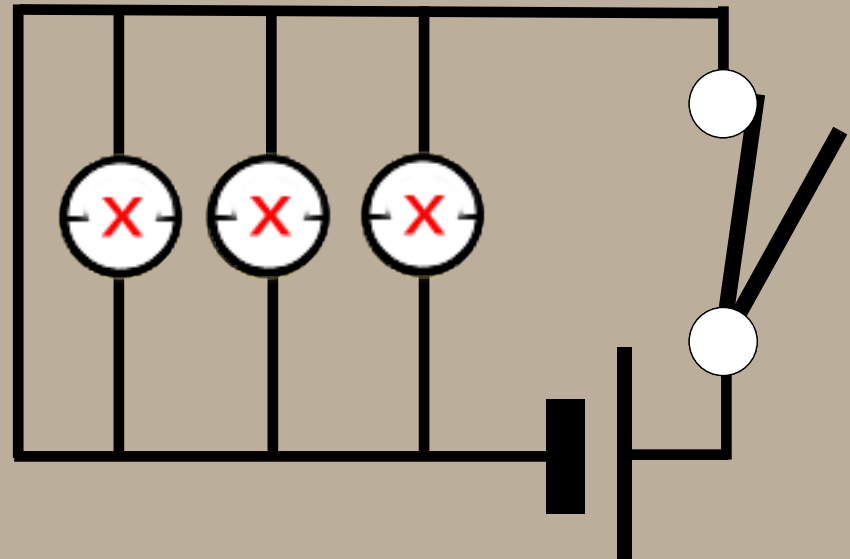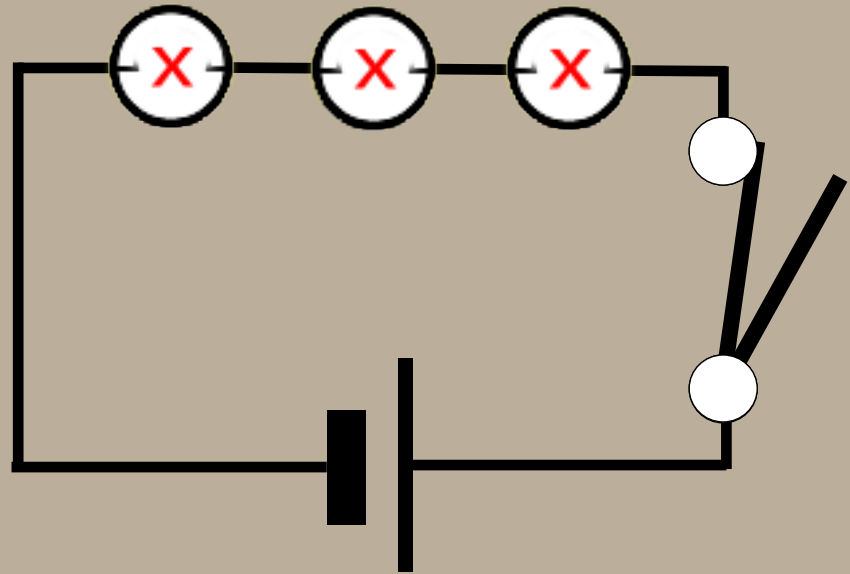Click elsewhere to proceed to next slide.



DIFFERENCES BETWEEN SERIES & PARALLEL CIRCUITS

Teacher Guide

Click to display
textboxes.

SERIES

If one globe burns out or is removed, all globes will stop working.

The voltage is shared between each globe, resulting in reduced brightness.

Serial circuits are cheap and easy to construct.

PARALLEL

If one globe burns out or is removed, all other globes will continue working.

Each globe receives the full voltage of the source, resulting in all globes burning at the same brightness regardless of the number of globes.

Parallel circuits require more effort to construct.


PREDICT WHAT WILL HAPPEN WHEN THE SWITCH IS

Teacher Guide

Click on the light switches to turn the globe on.

Nothing should happen.

Discuss short circuits.

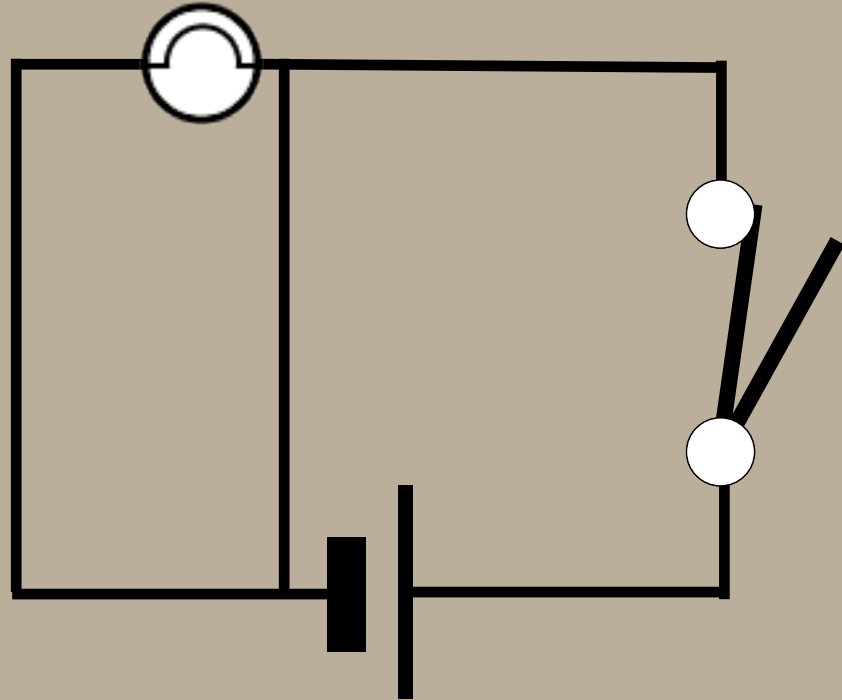


PREDICT WHAT WILL HAPPEN WHEN THE SWITCH IS

Teacher Guide

Click on the light switches to turn the globe off.

Nothing should happen.

on.

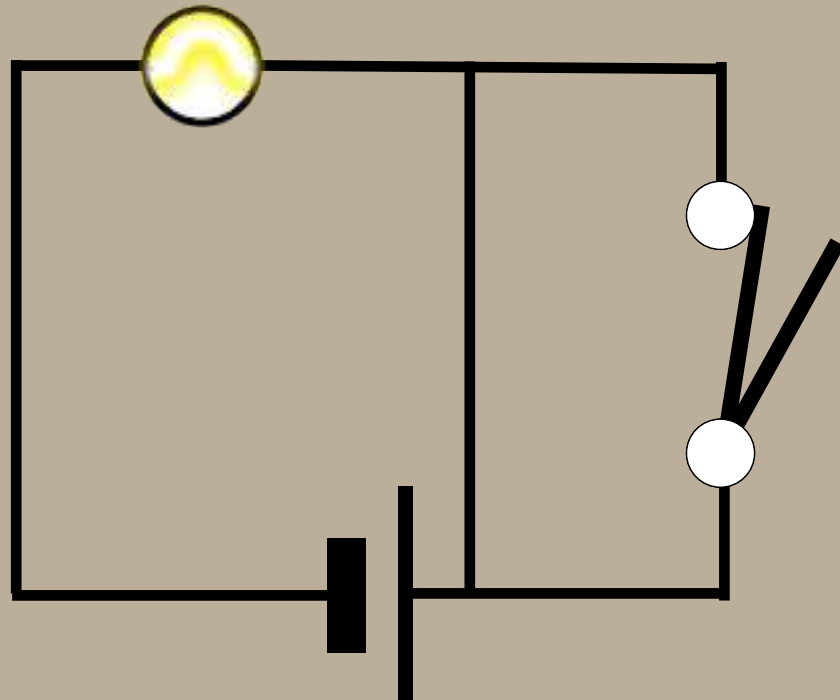


WHERE WOULD YOU FIND THIS CIRCUIT?

Teacher Guide

Click on the light switches to turn the globes on and off. Discuss household lighting circuits. Click elsewhere to proceed to next slide.

circuit with
individual
switches for
each light

Show Teacher Guide

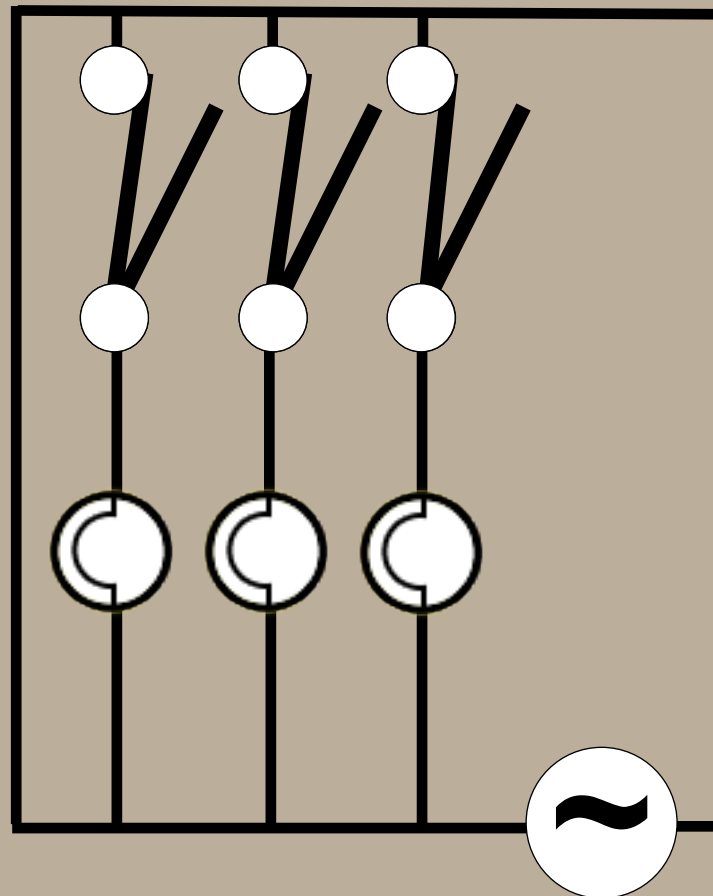

WHERE WOULD YOU FIND THIS CIRCUIT?


Teacher Guide

Click on the light switches to turn the globes on and off.

Safety switch will override all other switches.

but a safety switch can shut off all devices at once.

Show Teacher Guide

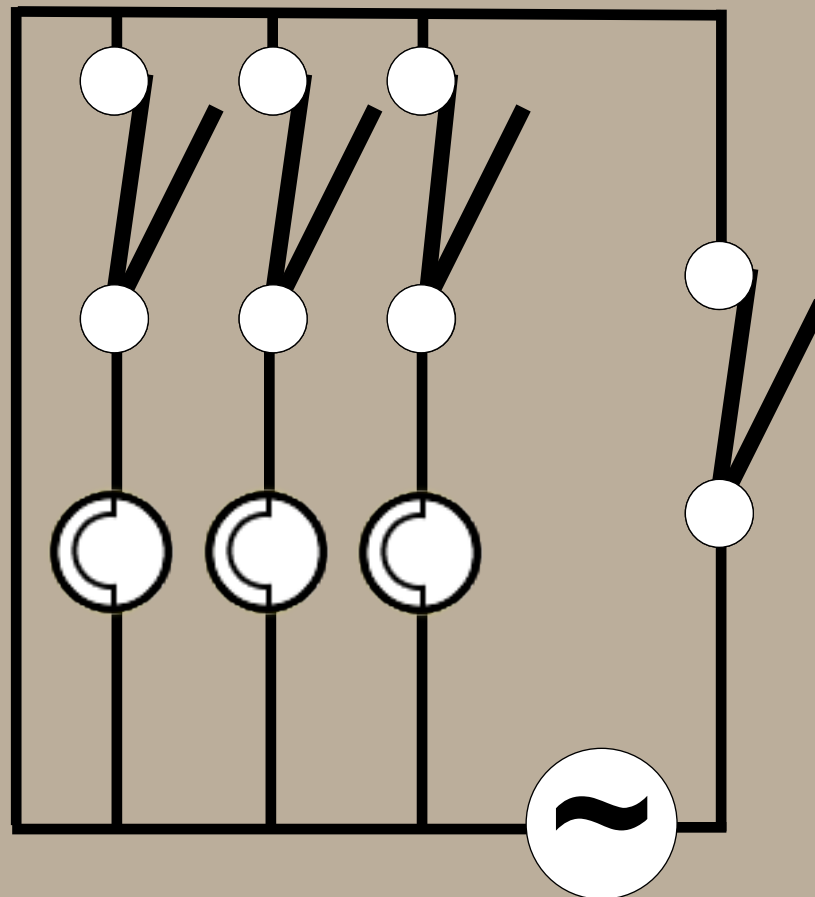

WHERE WOULD YOU FIND THIS CIRCUIT?


Teacher Guide

Click on the AC power source symbol to cycle through switching scenarios.

Click on slide to display image of staircase.

Discuss 2-way switches.

the stairs.

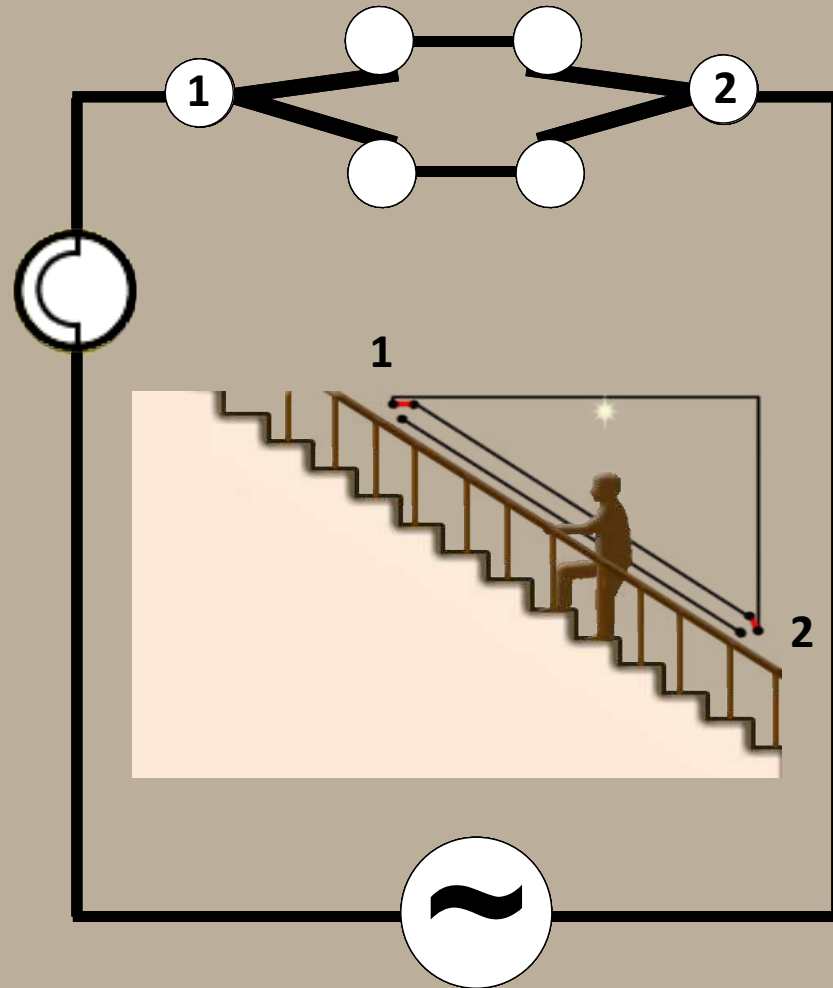

CHRISTMAS TREE LIGHTS SERIES OR PARALLEL

Teacher Guide

Click to fade Christmas tree
to reveal series circuit.

Click to show parallel
circuit.

Parallel



CHRISTMAS TREE LIGHTS SERIES

Teacher Guide

Click on slide to “break” a globe.
Note all globes do not work.



CHRISTMAS TREE LIGHTS PARALLEL

Teacher Guide

Repeatedly click on the
slide to break globes.

Note all other globes
remain working.

Repeat until all globes are
off.



ABOUT

This and other quality resources can be found on



Released by SciencePoint under



Attribution - NonCommercial - Share Alike
CC BY-NC-SA

This licence lets others distribute, remix and build upon the work, but only if it is for non-commercial purposes, they credit the original creator/s (and any other nominated parties) and they license their derivative works under the same terms.