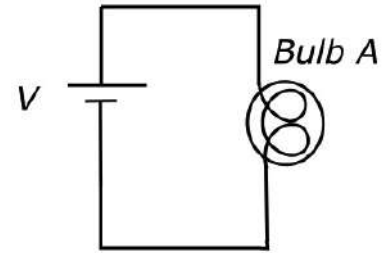


NAME \_\_\_\_\_


DATE \_\_\_\_\_

**Scenario**

A simple circuit is constructed with a single battery, wires, and a single bulb with resistance  $R$ .

**Quantitative Analysis**

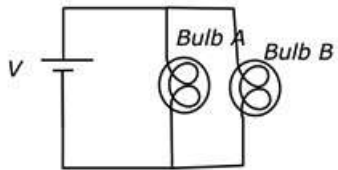**PART A:** When a second identical bulb (Bulb B) is placed in the circuit as shown below, describe what happens to the total resistance of the circuit. Provide evidence.




---




---



---

**PART B:** Write an expression for the total resistance of the circuit in terms of  $R$ , the resistance of a light bulb.

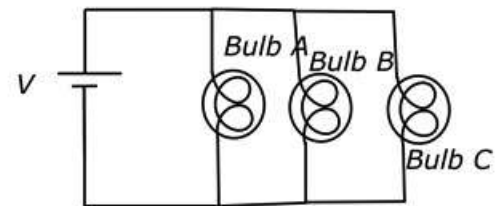**PART C:** A third identical bulb (Bulb C) is now added to the circuit. Fill in the following table to show what changes and what stays the same in each circuit after Bulb C is added in parallel. Place a check mark or an X in the correct box: increases, decreases, or remains the same.



	<i>Increases</i>	<i>Decreases</i>	<i>Remains the Same</i>
Total $\Delta V$			
$\Delta V$ (across Bulb A)			
$\Delta V$ (across Bulb B)			
Total Current			
Current through Bulb A			
Current through Bulb B			
Total Resistance			

### Analyze Data

**PART D:** The three bulbs are then taken out of the circuit and rearranged so that, with the switch closed, Bulb A is brighter than Bulbs B and C, and Bulbs B and C are equally bright.

With the switch open, Bulb A is off, and Bulbs B and C stay about the same brightness as when the switch was closed.

Sketch the circuit below.