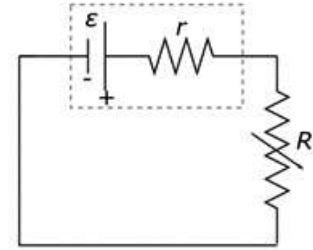


NAME \_\_\_\_\_

DATE \_\_\_\_\_

**Scenario**

A battery  $\varepsilon$  has internal resistance  $r$  and is connected to a variable resistor as shown.

**Quantitative Analysis****PART A:**

- i. As the resistance of the variable resistor is increased, which of the following quantities stays the same?

\_\_\_\_\_  $I$  \_\_\_\_\_  $\varepsilon$  \_\_\_\_\_  $r$  \_\_\_\_\_ All quantities stay the same.

- ii. As  $R$  is increased, does the potential difference measured across the battery increase, decrease, or remain the same? Explain.

\_\_\_\_\_ Increase \_\_\_\_\_ Decrease \_\_\_\_\_ Remains the same

---

---

---

---

---

---


---

**PART B:**

- i. Use Kirchhoff's loop rule to write an equation for the potential drops around the circuit in terms of  $\varepsilon$ ,  $I$ ,  $r$ , and  $R$ .

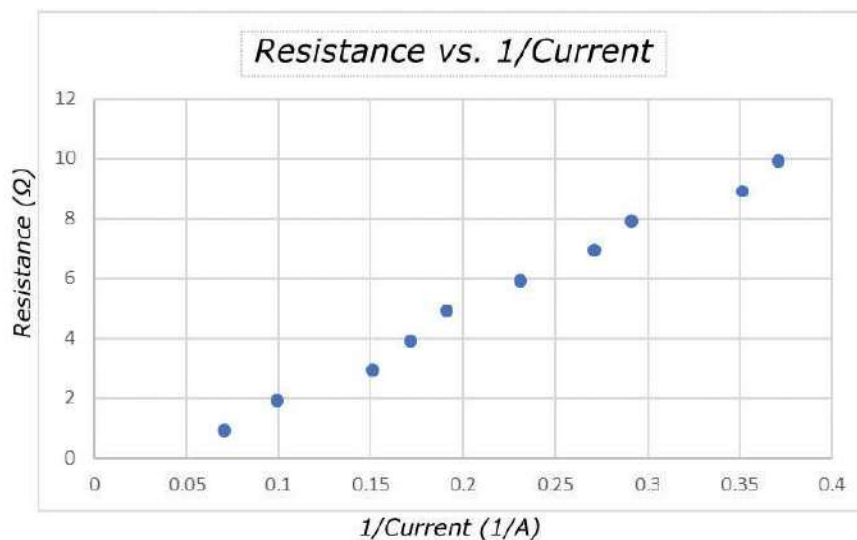- ii. Rewrite the equation from Part B (i) to solve for  $R$  as a function of  $I$ .

Dominique records the current through the variable resistor as a function of the resistance and collects the following data.



**PART D:** Draw a best-fit line and determine the slope.

---

---

**PART E:** What is the physical meaning of the slope?

---

**PART F:** Determine the  $y$ -intercept. What is the physical meaning of the  $y$ -intercept?

---

---

---

---