

NAME \_\_\_\_\_

DATE \_\_\_\_\_

**Scenario**

A power supply provides a constant potential difference  $\mathcal{E}$  but has internal resistance  $r$ . Angela wishes to build a light bulb and must select a resistance  $R$  for the light bulb. The resistance is determined when she cuts a filament to a certain length. She wishes to choose a value of  $R$  that will maximize the brightness (power  $P$  delivered to) the light bulb when it is connected to the power supply.

-----

**Using Representations**

**PART A:** Draw a circuit diagram showing the potential difference  $\mathcal{E}$ , resistor  $r$ , and light bulb  $R$ . Also draw a voltmeter and an ammeter that are correctly connected to measure the potential difference across and the current through the light bulb. Label all components.

**Analyze Data**

**PART B:** Angela cuts several different filaments of different resistances  $R$  and connects them individually to the power supply. She notices that very large values of  $R$  result in dim illumination (low  $P$ ) and very small values of  $R$  also result in dim illumination. Provide brief answers to the following questions in terms of current, potential difference, or both.

i. Why do high values of  $R$  result in low values of  $P$ ?

---



---



---

ii. Why do low values of  $R$  result in low values of  $P$ ?

---



---



---



---



---



---



---

**Quantitative Analysis**

**PART C:** Derive an expression for  $P$ , the power delivered to the light bulb, in terms of  $\varepsilon$ ,  $r$ , and  $R$ .


**PART D:**

- i. Show how your expression in Part C supports the idea that high values of  $R$  result in low values of  $P$ .

---

---

- ii. Show how your expression in Part C supports the idea that low values of  $R$  result in low values of  $P$ .

---

---

---

---

---

---

---

---

---

---