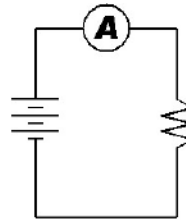


NAME _____


DATE _____

Scenario


Circuit 1 is connected at time $t = 0$ and the chemical reaction taking place within the battery reaches completion after 2 hours. The two graphs show the current passing through the battery and resistor as a function of time and the power delivered by the battery and to the resistor as a function of time.



Circuit 1

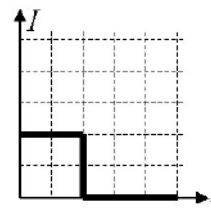


Circuit 1's I vs. t

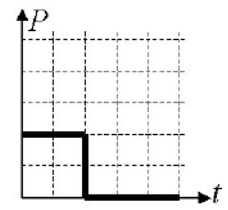


Circuit 1's P vs. t

Using Representations


PART A: Circuit 2 is shown below and has a fresh identical battery and identical resistors as Circuit 1. The I vs. t graphs and P vs. t graphs have the same scale as the corresponding graphs above. Sketch graphs of I and P for the battery as a function of time and graphs of I and P for one of the resistors as a function of time.

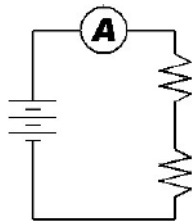


Circuit 2

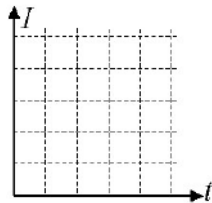


I vs. t for battery

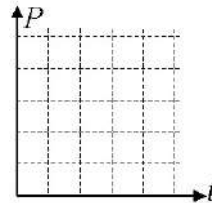

P vs. t for battery

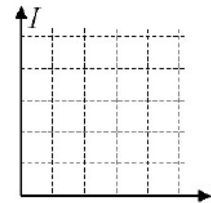


I vs. t for a resistor

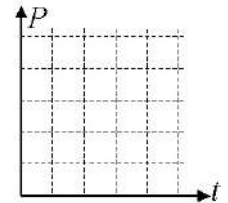

P vs. t for a resistor

Explain your reasoning for the graphs you constructed.

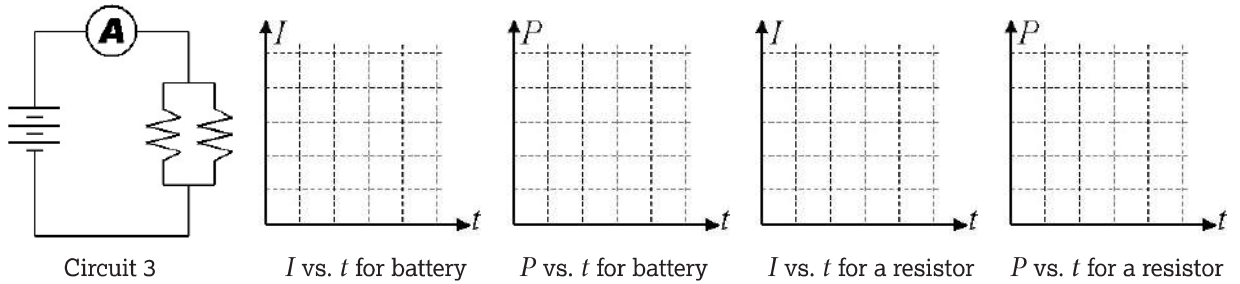PART B: Circuit 3 is shown below. It has a fresh identical battery and identical resistors as Circuit 1. The I vs. t graphs and P vs. t graphs have the same scale as the corresponding graphs above. Sketch graphs of I and P for the battery as a function of time and graphs of I and P for one of the resistors as a function of time.



Explain your reasoning for the graphs you constructed.

This image shows a single sheet of white paper with horizontal ruling lines. The lines are evenly spaced and run across the width of the page. There are no margins, text, or other markings on the paper.