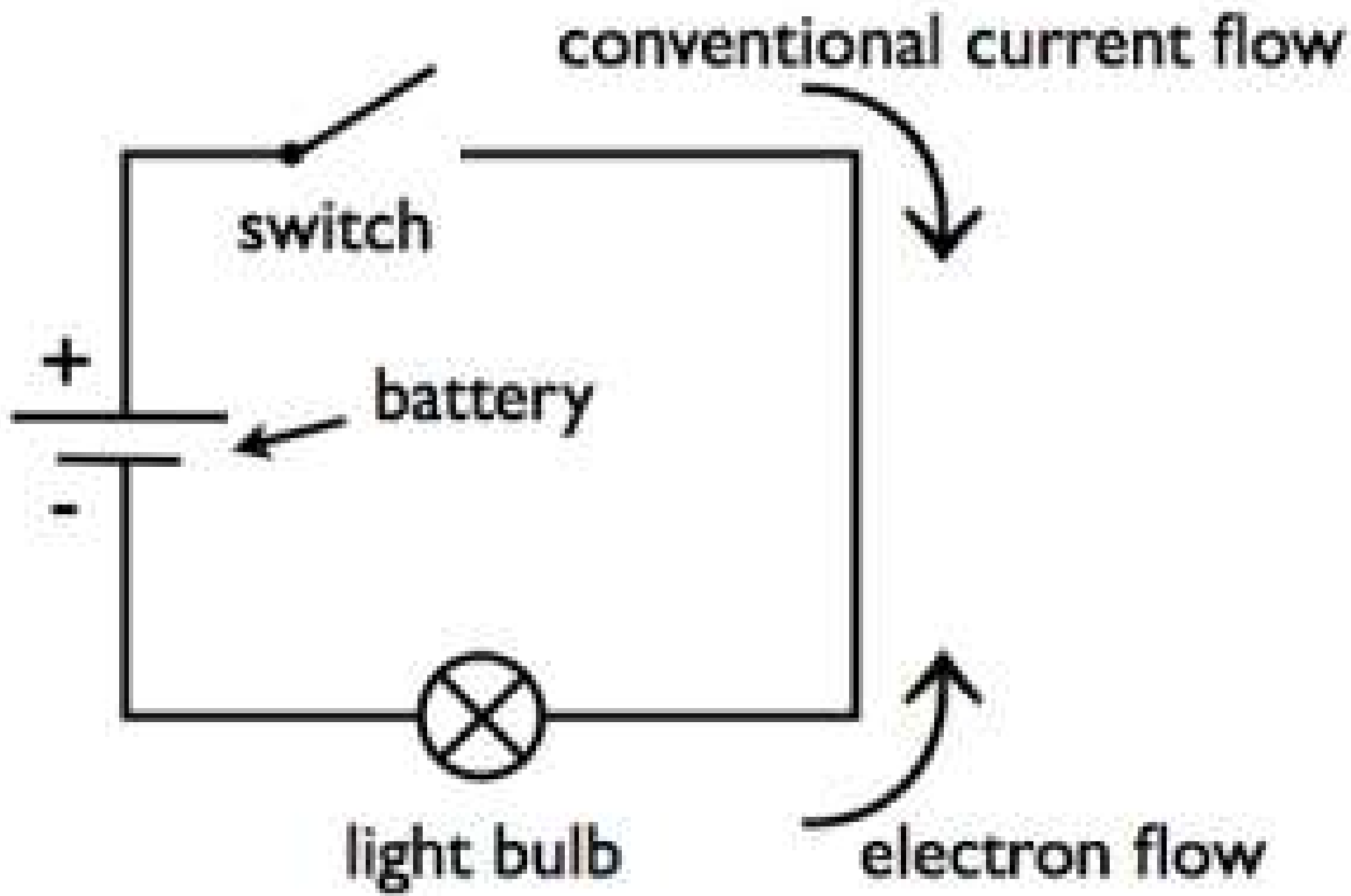


Chapter 17

◆ Circuits

Schematic Diagram

- ◆ A diagram that depicts the construction of an electrical apparatus is called a schematic diagram.
- ◆ Diagrams use symbols to represent bulbs, batteries, and wires.




Electric Circuit

- ◆ Together, the bulb, battery, switch, and wire form the electric circuit.
- ◆ This is a path through which charges can flow.

Short Circuits

- ◆ In a short circuit, the current can increase and become unsafe.
- ◆ The wires can't withstand the increased current, and begin to overheat.

Short Circuit Demo

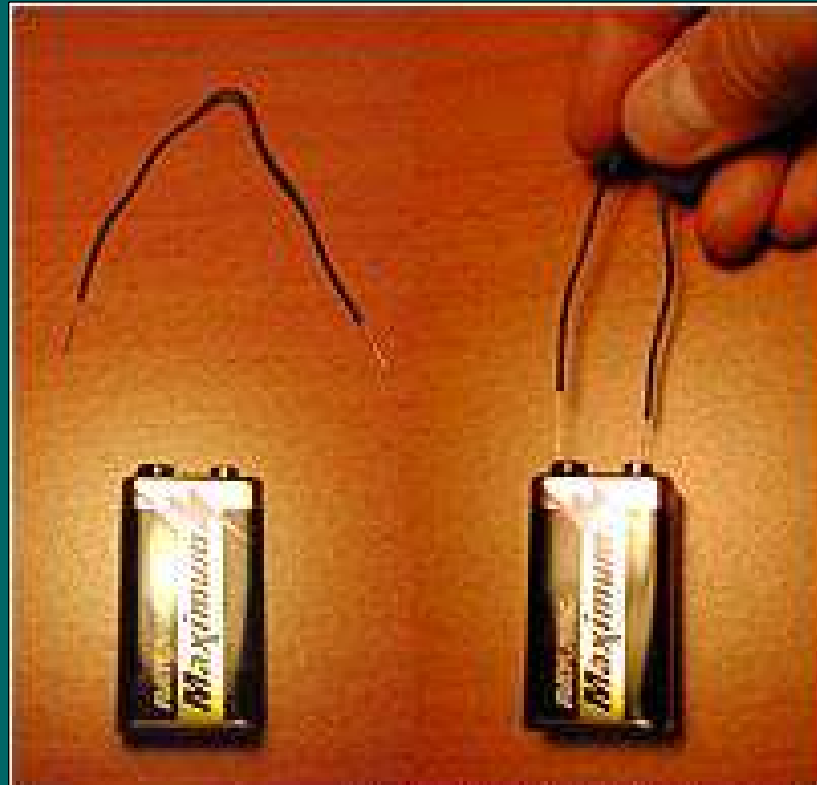


Copyright PhysLink.com

Image: The simplest example of a 'Short Circuit'. All you need is a battery and a piece of wire. If you do this in dark you may notice faint sparking when you connect + to - of the battery.

Resistors in Series

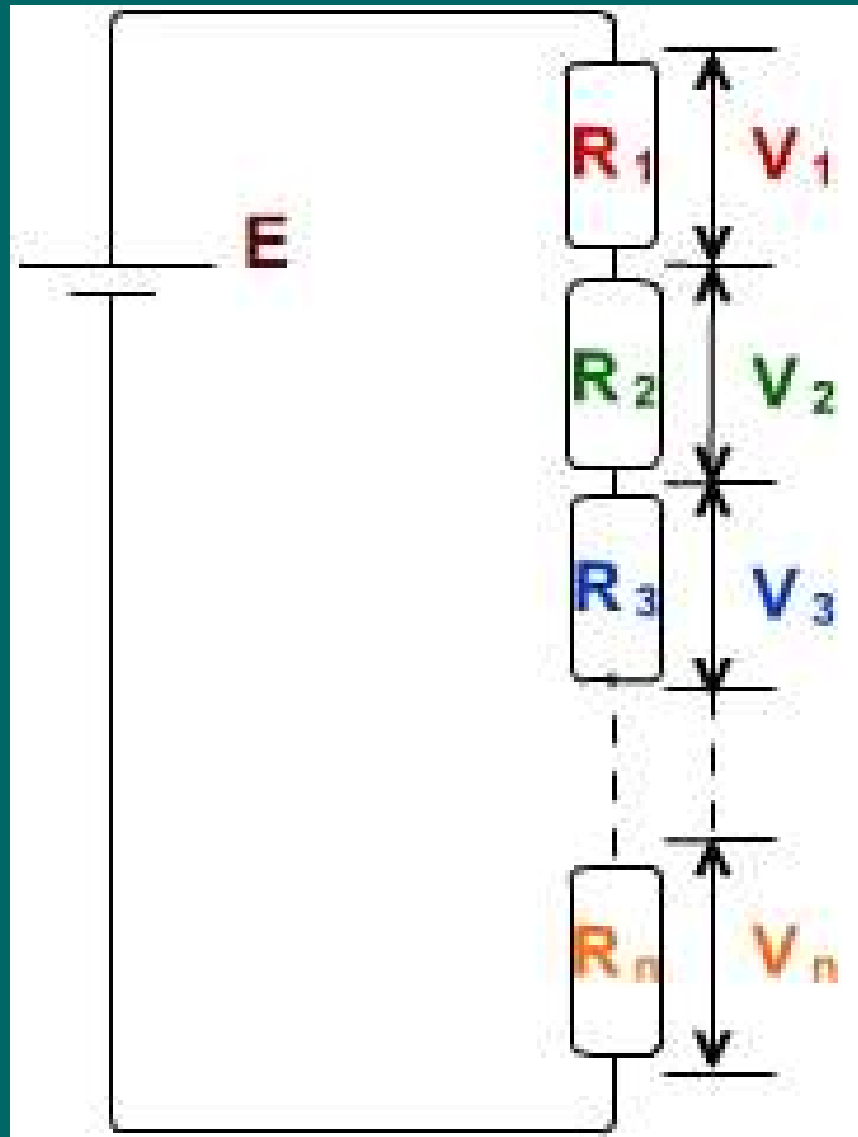- ◆ In series, there is only one path for the current to flow.
- ◆ When many resistors are connected in series, the current in each resistor is the same.
- ◆ $R_1 + R_2 + \dots = R_{\text{total}}$




A 9 V battery is connect to 4 bulbs with resistance of 2, 4, 5, and 7. What is the current of the circuit?

◆ Current = V / R_{Total}

Resistance in Parallel

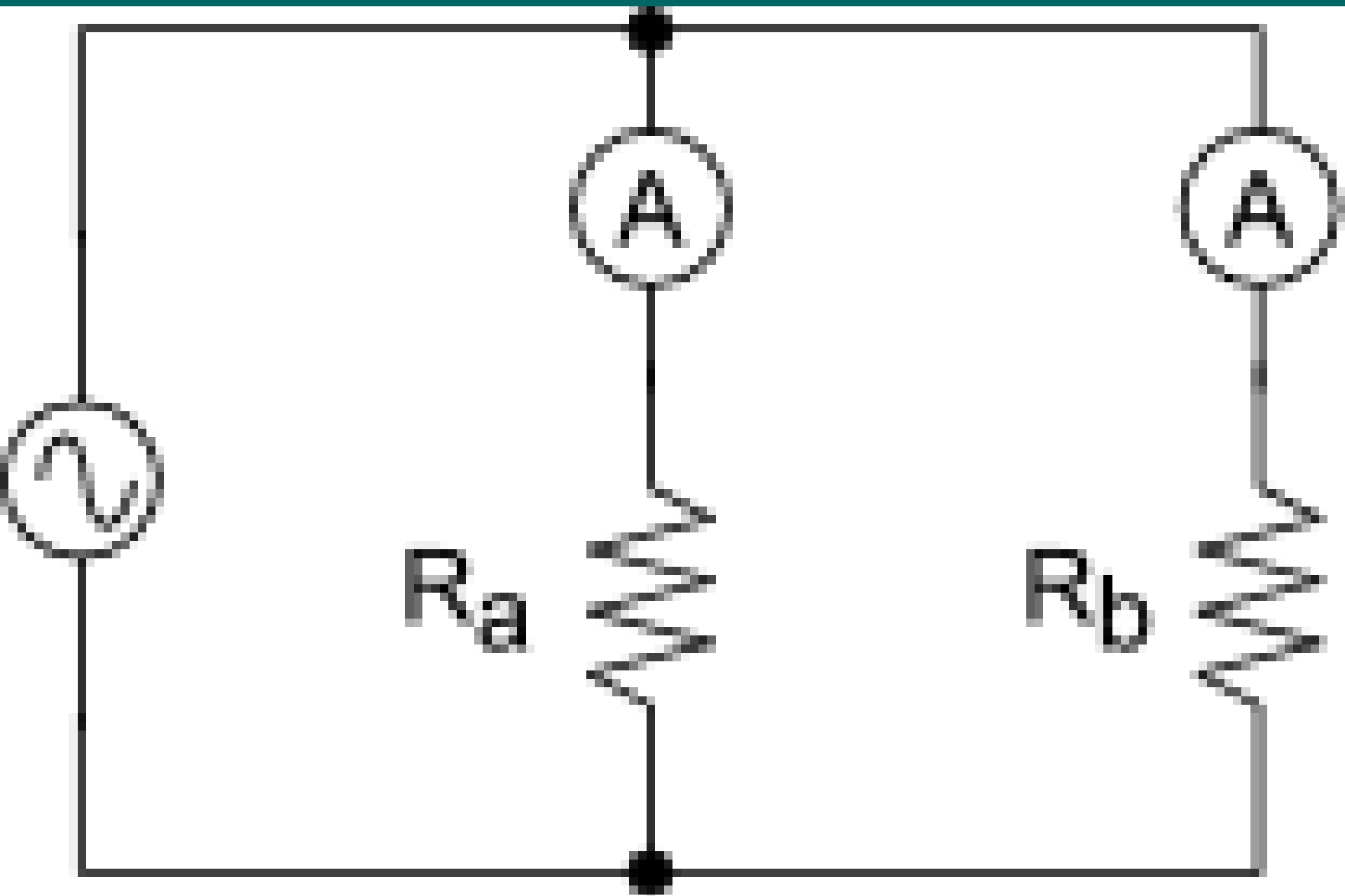- ◆ Parallel means there are more than 1 path for a current to flow.
- ◆ $1/R_{\text{total}} = 1/R_1 + 1/R_2 \dots$



A 9 V battery is connected to 4 resistors connected in parallel. The resistors are 2, 4, 5, and 7. What is the current?

◆ Current = V / R