# Circuit Virtual Escape Room Map ~ [3-Player]

Welcome Player 1...

You must work with your team to earn your reward Your clues interact, and you cannot afford To leave groupmates behind or sit silently staring This is time for unmuting and time for screen sharing.

This escape room requires your circuitry smarts You will face separate doors and will have unique parts Of the overall challenge. It will test your persistence As you calculate voltage, current, power, resistance

Make sure that you're careful and read all the text When your team is all ready, you can start - just click "Next" Welcome Player 2...

You must work with your team to earn your reward Your clues interact, and you cannot afford To leave groupmates behind or sit silently staring This is time for unmuting and time for screen sharing.

This escape room requires your circuitry smarts You will face separate doors and will have unique parts Of the overall challenge. It will test your persistence As you calculate voltage, current, power, resistance

Make sure that vou're careful and read all the text When your team is all ready, you can start - just click "Next" Welcome Player 3...

You must work with your team to earn your reward Your clues interact, and you cannot afford To leave groupmates behind or sit silently staring This is time for unmuting and time for screen sharing.

This escape room requires your circuitry smarts You will face separate doors and will have unique parts Of the overall challenge. It will test your persistence As you calculate voltage, current, power, resistance

Make sure that you're careful and read all the text When your team is all ready, you can start - just click "Next"

The resistor shown below has a 3-watt power rating From this published limit, find volts by calculating Maximum voltage for the resistance shown by colors Too bad your data's scrambled, compare lists with all the others

The resistor shown below has a 3-watt power rating From this published limit, find volts by calculating Maximum voltage for the resistance shown by colors Too bad your data's scrambled, compare lists with all the others

The resistor shown below has a 3-watt power rating From this published limit, find volts by calculating Maximum voltage for the resistance shown by colors Too bad your data's scrambled, compare lists with all the others



Resistance =  $3 \Omega$ 



Resistance =  $75 \Omega$ 



Resistance =  $10 \Omega$ 

Brown - Black - Black

Mass: 15 g Diameter: 5.5 mm Length: 15.0 mm Resistance:  $10 \Omega$ Power Rating: 3 W

Operating Temperature: -55°C ~ 235°C

https://www.digikey.com/en/products/detail/stackpoleelectronics-inc/RSMF3JT10R0/1695561

Orange - Black - Gold

Mass: 15 a Diameter: 5.5 mm Length: 15.0 mm Resistance: 3  $\Omega$ Power Rating: 3 W

Operating Temperature: -55°C ~ 235°C

https://www.digikey.com/en/products/detail/stackpole-

electronics-inc/RSMF3JT3R00/1695451

Purple - Green - Black

Mass: 15 g Diameter: 5.5 mm Length: 15.0 mm Resistance:  $75 \Omega$ Power Rating: 3 W

Operating Temperature: -55°C ~ 235°C


https://digikey.com/en/products/detail/stackpole-electronics-

inc/RSMF3JT75R0/1695621

3 V

15 V

5.477 V (5.4-5.5)

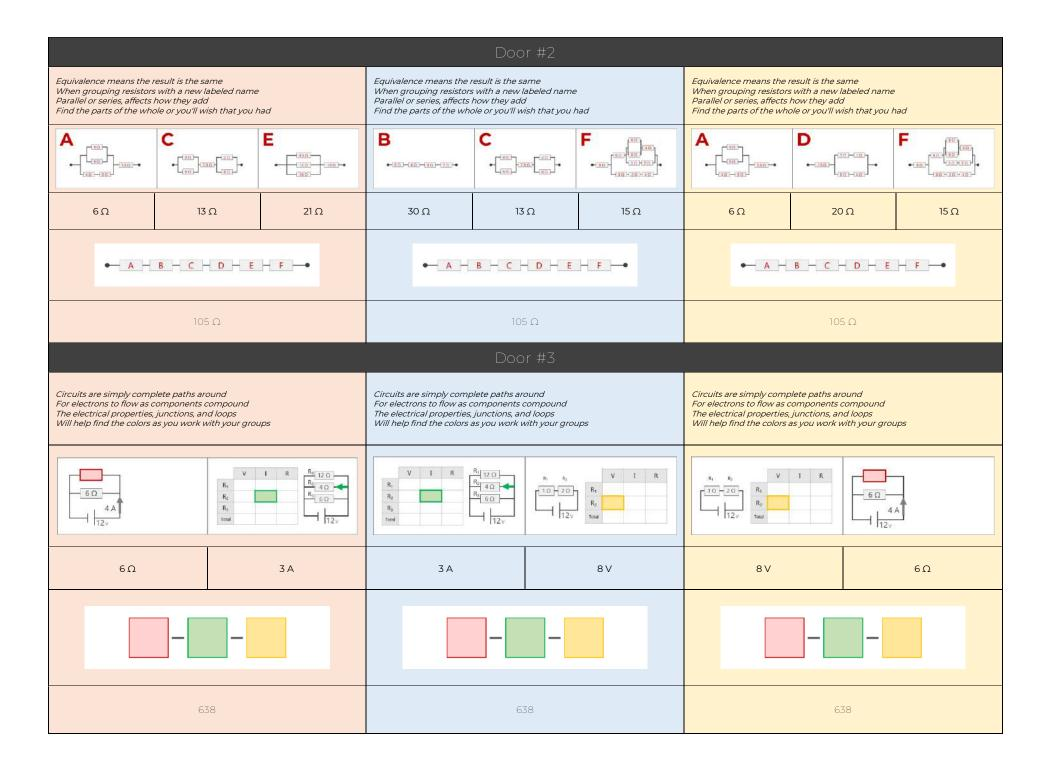

| Door #4   |   |   |
|---|---|---|
| This next door is different it's kind of a maze<br>You're all an electron that can move different ways<br>At each junction, one person is given a clue<br>Take their advice or be back for round two. | This next door is different it's kind of a maze<br>You're all an electron that can move different ways<br>At each junction, one person is given a clue<br>Take their advice or be back for round two. | This next door is different it's kind of a maze<br>You're all an electron that can move different ways<br>At each junction, one person is given a clue<br>Take their advice or be back for round two.       |
| $7\Omega$ $9\Omega$ $8\Omega$ $6\Omega$ $3\Omega$ $5\Omega$ $8\Omega$ $9\Omega$ $9\Omega$ $9\Omega$ $9\Omega$ $9\Omega$ $9\Omega$ $9\Omega$ $9$   | A $A$ $B$ $A$ $B$ $A$ $B$   | $7\Omega$ $9\Omega$ $8\Omega$ $6\Omega$ $3\Omega$ $5\Omega$ $8\Omega$ $9\Omega$ $9\Omega$ $9\Omega$ $9\Omega$ $9\Omega$ $9\Omega$ $9\Omega$ $9$   |
| You must know the charge that electrons all carry<br>Since "like repels like" as discussed<br>In schematics we know that the batteries can vary<br>But the long line is always the plus               | А   | А   |
| В   | With where you sit now there are multiple "halls" They are labeled with A, B, and C Pick the branch where resistance is smallest in all To make the right choice of these three                       | В   |
| А   | А   | Each choice that you see has three different resistors<br>Connected in two different ways<br>Pick the one where the current ain't the same for all sisters<br>And you'll continue to move through this maze |
| The voltage that's used is the same for each path But in one the flow is much slower The current is found with quite simple math Is the slow one the upper or lower?                                  | В   | В   |
| 7 Ω   | When this mess of a circuit is connected and flowing<br>The voltage supplied is eighteen<br>Which resistor to choose? The key is in knowing<br>Where "ten and a half" volts are seen                  | 7 Ω   |

|   | Door #5  |   |
|---|--|---|
| You reach in your backpack and pull out a wire<br>To get through this next door, you'll see I require<br>The name of the metal, and for your calculation<br>Each member has some of the right information | You reach in your backpack and pull out a wire<br>To get through this next door, you'll see I require<br>The name of the metal, and for your calculation<br>Each member has some of the right information  | You reach in your backpack and pull out a wire<br>To get through this next door, you'll see I require<br>The name of the metal, and for your calculation<br>Each member has some of the right information |
| 200 Pt  | A A A A A A A A A A A A A A A A A A A  | 4 mm  |
| The spool of wire is labeled "200 ft". Convert this into meters.  | You hook up the wire to a potential difference of 3 volts and<br>measure 5.83 A with an ideal ammeter.   | What is the cross-sectional area of the wire?<br>Complete the missing value rounded to 2 decimal places   |
| 60.96 m   | 0.515 (0.514-0.515)  | 1.26 × 10 <sup>-5</sup> (1.25-1.26)   |
| Material   Resistivity  | Material         Resistivity           Silver         1.59 × 10 ° Ωm           Copper         1.68 × 10 ° Ωm           Gold         2.44 × 10 ° Ωm           Aluminum         2.65 × 10 ° Ωm           Tungsten         5.6 × 10 ° Ωm           Iron         9.71 × 10 ° Ωm           Platinum         1.06 × 10 ° Ωm           Manganin         4.82 × 10 ° Ωm           Lead         2.2 × 10 ° Ωm           Mercury         9.8 × 10 ° Ωm           Nichrome         1.0 × 10 ° Ωm           Constantan         49 × 10 ° Ωm           Quartz (fused)         7.5 × 10 ° Γ αm | Material   Resistivity  |
| $ ho = rac{RA}{L}$ Resistivity is a property that can help define the material   | $ ho = rac{RA}{L}$ Resistivity is a property that can help define the material  | $ ho = rac{RA}{L}$ Resistivity is a property that can help define the material   |
| What is the wire made of?   | What is the wire made of?  | What is the wire made of?   |
| Platinum  | Platinum   | Platinum  |

### Door #6

This final door's equipped with two factor authentication To get your final clue, I need a little communication This crazy awesome circuit gives a crucial little digit Incorporate it wisely and you'll soon receive your ticket


Just looking at those branches sends my mind into twisters I'll save you the counting, there are 25 resistors.

This final door's equipped with two factor authentication To get your final clue, I need a little communication This crazy awesome circuit gives a crucial little digit Incorporate it wisely and you'll soon receive your ticket

Just looking at those branches sends my mind into twisters I'll save you the counting, there are 25 resistors.

This final door's equipped with two factor authentication To get your final clue, I need a little communication This crazy awesome circuit gives a crucial little digit Incorporate it wisely and you'll soon receive your ticket

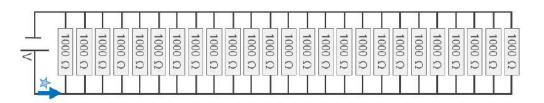Just looking at those branches sends my mind into twisters I'll save you the counting, there are 25 resistors.



Someone has an address with a star in the middle Replace it with the current to receive your final riddle If the current is your goal, total volts is good to get It's the same amount of voltage as a standard US outlet Send an email message if you want to move on Circuitescape\*@gmail.com

Email circuitescape3@gmail.com

#### Your next Clue:


You found circuit success since you knew where to send You must answer this riddle to get to the end What did the announcer say when the resistor hit the baseball out of the park?


\_\_\_\_!!


Ohm run
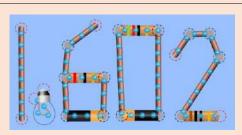
## CONGRATULATIONS!!

You made it to the end and the feeling is ELECTRIC! It's clear your group is ready, you accomplished every metric Share this code here with your teacher to prove that you are done I hope this helped review things and I hope that you had fun You made it to the end and the feeling is ELECTRIC! It's clear your group is ready, you accomplished every metric Share this code here with your teacher to prove that you are done I hope this helped review things and I hope that you had fun You made it to the end and the feeling is ELECTRIC! It's clear your group is ready, you accomplished every metric Share this code here with your teacher to prove that you are done I hope this helped review things and I hope that you had fun



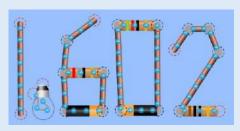

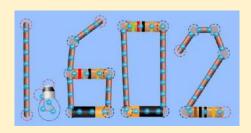

| Submit Form   |   |   |  |
|---|---|---|--|
| Congratulations again!!   | Congratulations again!!   | Congratulations again!!   |  |
| 1.602 isn't just a random code you know. It's a reference to the elementary charge of protons on electrons (1.60217662 x 10^-19 Coulombs) | 1.602 isn't just a random code you know. It's a reference to the elementary charge of protons on electrons (1.60217662 x 10^-19 Coulombs) | 1.602 isn't just a random code you know. It's a reference to the elementary charge of protons on electrons (1.60217662 x 10^-19 Coulombs) |  |
| Electricity all the way through :)  | Electricity all the way through :)  | Electricity all the way through:)   |  |