

Circuits Assessment

Station 1

Determine the equivalent resistance using the color bands.



COLOR	1 ST BAND	2 ND BAND	3 RD BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1 Ω	
Brown	1	1	1	10 Ω	\pm 1% (F)
Red	2	2	2	100 Ω	\pm 2% (G)
Orange	3	3	3	1K Ω	
Yellow	4	4	4	10K Ω	
Green	5	5	5	100K Ω	\pm 0.5% (D)
Blue	6	6	6	1M Ω	\pm 0.25% (C)
Violet	7	7	7	10M Ω	\pm 0.10% (B)
Grey	8	8	8	100M Ω	\pm 0.05%
White	9	9	9	1G Ω	
Gold				0.1 Ω	\pm 5% (J)
Silver				0.01 Ω	\pm 10% (K)





COLOR	1 ST BAND	2 ND BAND	3 RD BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1 Ω	
Brown	1	1	1	10 Ω	\pm 1% (F)
Red	2	2	2	100 Ω	\pm 2% (G)
Orange	3	3	3	1K Ω	
Yellow	4	4	4	10K Ω	
Green	5	5	5	100K Ω	\pm 0.5% (D)
Blue	6	6	6	1M Ω	\pm 0.25% (C)
Violet	7	7	7	10M Ω	\pm 0.10% (B)
Grey	8	8	8	100M Ω	\pm 0.05%
White	9	9	9	1G Ω	
Gold				0.1 Ω	\pm 5% (J)
Silver				0.01 Ω	\pm 10% (K)





Station 2

Create a circuit diagram for each circuit.

Station 3

Create the circuit diagram provided by your teacher. After you build each one, get it checked by your teacher.

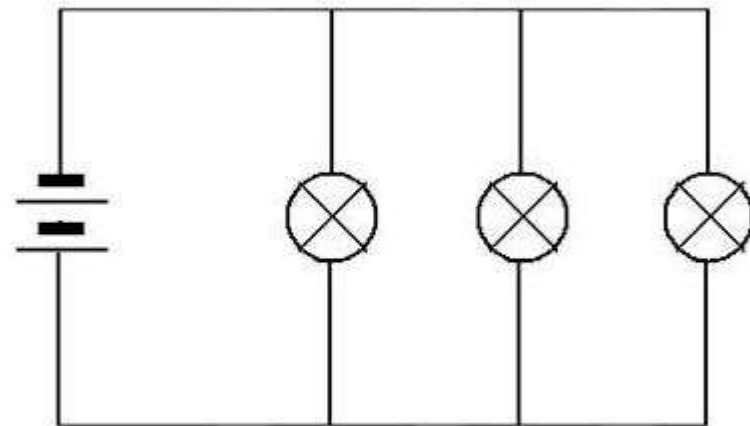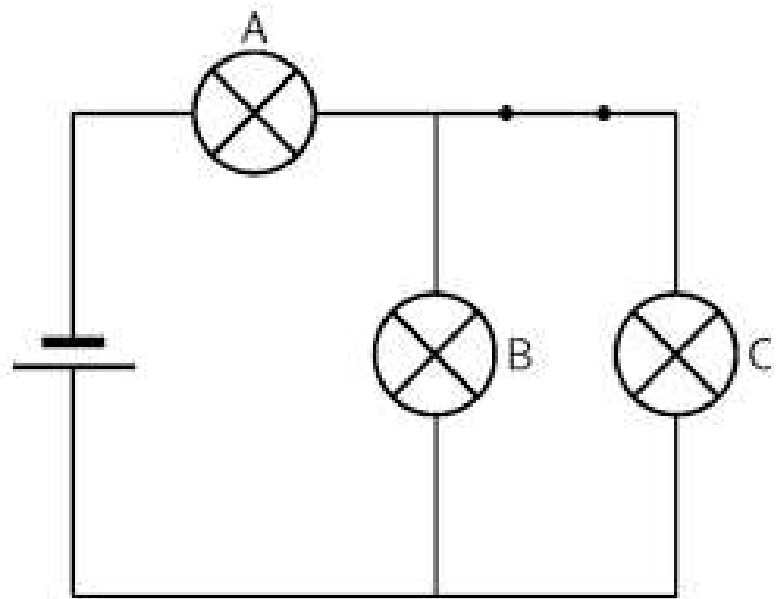

Station 4

Create a circuit diagram for each circuit and compare and contrast the configuration and brightness of the circuits.

Station 5

Determine the current
assuming the voltage is 10
volts.



COLOR	1 ST BAND	2 ND BAND	3 RD BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1 Ω	
Brown	1	1	1	10 Ω	\pm 1% (F)
Red	2	2	2	100 Ω	\pm 2% (G)
Orange	3	3	3	1K Ω	
Yellow	4	4	4	10K Ω	
Green	5	5	5	100K Ω	\pm 0.5% (D)
Blue	6	6	6	1M Ω	\pm 0.25% (C)
Violet	7	7	7	10M Ω	\pm 0.10% (B)
Grey	8	8	8	100M Ω	\pm 0.05%
White	9	9	9	1G Ω	
Gold				0.1 Ω	\pm 5% (J)
Silver				0.01 Ω	\pm 10% (K)





COLOR	1 ST BAND	2 ND BAND	3 RD BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1 Ω	
Brown	1	1	1	10 Ω	\pm 1% (F)
Red	2	2	2	100 Ω	\pm 2% (G)
Orange	3	3	3	1K Ω	
Yellow	4	4	4	10K Ω	
Green	5	5	5	100K Ω	\pm 0.5% (D)
Blue	6	6	6	1M Ω	\pm 0.25% (C)
Violet	7	7	7	10M Ω	\pm 0.10% (B)
Grey	8	8	8	100M Ω	\pm 0.05%
White	9	9	9	1G Ω	
Gold				0.1 Ω	\pm 5% (J)
Silver				0.01 Ω	\pm 10% (K)



Station 6

Each light has a resistance of 15 Ohms. Determine the equivalent resistance and the current assuming the voltage is 10V.