

$$I = \frac{\Delta q}{\Delta t}$$

I = Current (in Amperes, Amps, A or C/s)

Δq = Charge that passes a point (C)

Δt = Time it takes charge to pass (s)

Example: What charge passes a certain point if a current of 250 mA flows for 12 minutes?

Whiteboards:

<p>1. What is the current flowing if 13.5 C goes through a light bulb in 7.5 seconds? (1.8 A)</p>	<p>2. What charge passes a certain point if you have a current of 2.10 A for 45.0 seconds (94.5 C)</p>
<p>3. What time will it take 65 C of charge to flow if you have a current of 120 mA? (540 s)</p>	<p>4. How much charge in 2.5 Amp Hours? (1 amp hour = 1 amp flowing for 1 hour) (9000 C)</p>

$$R = \frac{V}{I}$$

R = Resistance in ohms (Ω)

V = Voltage in Volts (V) (pressure)

I = Current in Amps (A) (flowrate)



Example 1: What is the resistance in the circuit above?


Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Gray	8
White	9
Gold	5%
Silver	10%
No color	20%

First digit
Second digit
Multiplier
Tolerance

Example 2: If there is a 220Ω resistor in the circuit above, what is the current?

Whiteboards:

1. What is the resistance of a light bulb if it draws 250 mA of current from a 6.15 V battery? (1000 mA = 1 A) (24.6Ω)	2. What current will flow if you plug a paperclip with a resistance of 0.065Ω into a 12 V source? (180 A)
3. What voltage do you need to push 1.5 Amps of current through a 210 ohm resistor? (315 V)	4. What current flows through an 8.1 ohm speaker when there is a voltage of 3.45 V? (0.43 A)
5. An unknown resistor draws 0.0128 Amps of current from a 23.9 V source. What is the resistance? (1870Ω)	6. A 1200 ohm resistor is hooked up to an unknown voltage source, and it draws 87.5 mA of current. What is the voltage? (105 V)

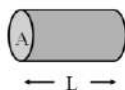

$$R = \frac{\rho L}{A}$$

$$\rho = \frac{RA}{L}$$

ρ - Resistivity in Ωm

L - Length of the wire in m

A - Cross sectional area of the wire (πr^2 ?)

R - Resistance of the wire in Ohms

Demo: Different wires

Some values of ρ in Ωm at 20°C
(From table 18-1 on p 535)

Silver	1.59E-8
Copper	1.68E-8
Gold	2.44E-8
Aluminium	2.65E-8
Tungsten	5.6 E-8
Iron	9.71E-8
Platinum	10.6E-8
Nichrome (alloy of Ni, Fe, Cr)	100E-8


Ex #1: A steel wire is 2.7 m long, and has a resistance of 7.3 ohms. What is its diameter?

Whiteboards:

1. A copper wire is 1610 m long (1 mile) and has a cross sectional area of $4.5 \times 10^{-6} \text{ m}^2$. What is its resistance? (This wire is about 2.4 mm in dia)
(6.0 Ω)

2. An Aluminium wire is 3.2 mm in diameter, and has a resistance of 142 ohms. What length is it?
(43,000 m)

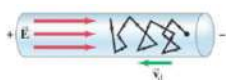3. A piece of wire has a diameter of 0.42 mm, and a length of 53 cm. What is its resistivity if it has a resistance of 4.9 ohms? (what kind of wire is it?) ($130 \times 10^{-8} \Omega\text{m}$)



$$I = nAvq$$

n – Number of charge carriers per m^3 (electrons m^{-3})

A – Cross sectional area of the wire (m^2) (πr^2 ?)

v – Electron drift speed (m/s)

q – Charge on one charge carrier (C)

Ex #1: A 2.4 mm diameter copper ($n = 8.5 \times 10^{28}$ carriers/ m^3) wire has a current of 5.8 amps flowing down it. What is the electron drift speed? (9.4×10^{-5} m/s)

Whiteboards:

<p>1. A 1.8 mm diameter copper ($n = 8.5 \times 10^{28}$ carriers/m^3) wire has an electron drift speed of 0.082 mm/s. What is the current flowing in the wire? (2.8 Amps)</p>	<p>2. A 3.4 mm wire of some material has an electron drift velocity of 0.016 mm/s when a current of 12 A flows. What is the density of charge carriers per cubic meter? (5.2×10^{29} carriers/m^3)</p>
<p>3. A copper ($n = 8.5 \times 10^{28}$ carriers/m^3) wire carrying 4.5 A has an electron drift speed of 0.13 mm/s. What is the diameter of the wire? (1.8 mm - 1.8×10^{-3} m)</p>	

$$P = VI = I^2R = \frac{V^2}{R}$$

P: Power in W

I: Current in Amps

V: Voltage in Volts


R: Resistance in Ohms

Example 1: If a car stereo uses 850 Watts of power, how many Amps does it use at 12 V?

Example 2: If you have 128 mA of current running through a 560 ohm resistor, what power will it dissipate, and what is the voltage across it?

Whiteboards:

1. A heating element draws 2.07 A from a 12.0 volt source. What is the power it consumes? (24.8 W)	2. What is the current flowing in a 75 W light bulb connected to 120 V? (0.625 A)
3. What is the power used by a 0.135 ohm heating element connected to a 24.0 V source? (4270 W)	4. A 345 mW light bulb draws 12.8 mA of current. What is its resistance? (2110 Ω)
5. A 0.25 Watt 1000. ohm resistor can be connected to what maximum voltage? (16 V)	6. What maximum current can flow through a 50.0 ohm resistor that is rated at 10.0 Watts? (447 mA)

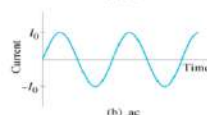

Concept 0

$$V = V_0 \sin(2\pi ft)$$

$$I = I_0 \sin(2\pi ft)$$

$$V_0 = \text{Peak } V$$

$$I_0 = \text{Peak } I$$

Demo - oscilloscope - what is our V_0 ???



$$P = I^2 R = V^2 / R$$

What Is "effective" I and V?

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$



$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$$

rms = root mean square

V_{rms} and I_{rms} is default - meters

If people mean "peak", they will say "peak"

What is our rms on the 'scope'?

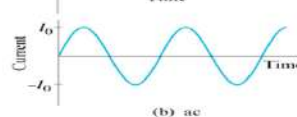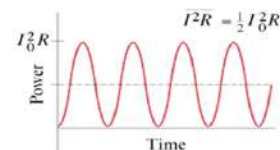

$$\bar{P} = \frac{1}{2} I_0 V_0$$

$$\text{Average Power} = \frac{1}{2} I_0^2 R = \frac{1}{2} V_0^2 / R$$

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$$

$$R = \frac{V_0}{I_0} = \frac{V_{\text{rms}}}{I_{\text{rms}}}$$

$$P_{\text{max}} = I_0 V_0$$

$$\bar{P} = \frac{1}{2} I_0 V_0$$

Example - A 13.50 ohm resistor has a peak voltage of 207.0 Volts across it. What is the rms voltage across it, and what is the peak and rms current through it, and the average power and peak power that it dissipates


Whiteboards:


1. What is the rms voltage if the peak voltage is 340 V? (240 V)

2. A circuit has an rms current of 1.45 A. What is the peak current? (2.05 A)

(Do the ones on the back too)

More Whiteboards: (What a good student you are!!)

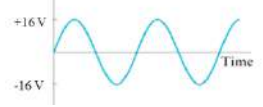
<p>3. What's the rms voltage here?</p> 	<p>4. What is the peak voltage if the rms voltage is 12 V? (17 V)</p>
<p>5. An 60.0 V alternating current is attached to a device that draws 3.5 amps. What is the power used? (210 W)</p>	<p>6. An alternating current with a peak voltage of 18.5 V is connected to a 27.5 ohm resistor. What power is dissipated? (6.22 W)</p>
<p>7. A 40. Watt light is connected to a 120 Volt source. What is the peak current through the light bulb, its resistance, and what is the peak power that it dissipates? (0.47 A, 360 ohms, 80. W)</p>	<p>8. A 100.2 ohm heating element is dissipating 1530 W of power. What are the peak current and peak voltage through and across the element? (find rms...) What is the peak power? (5.5 A, 554 V, 3060 W)</p>

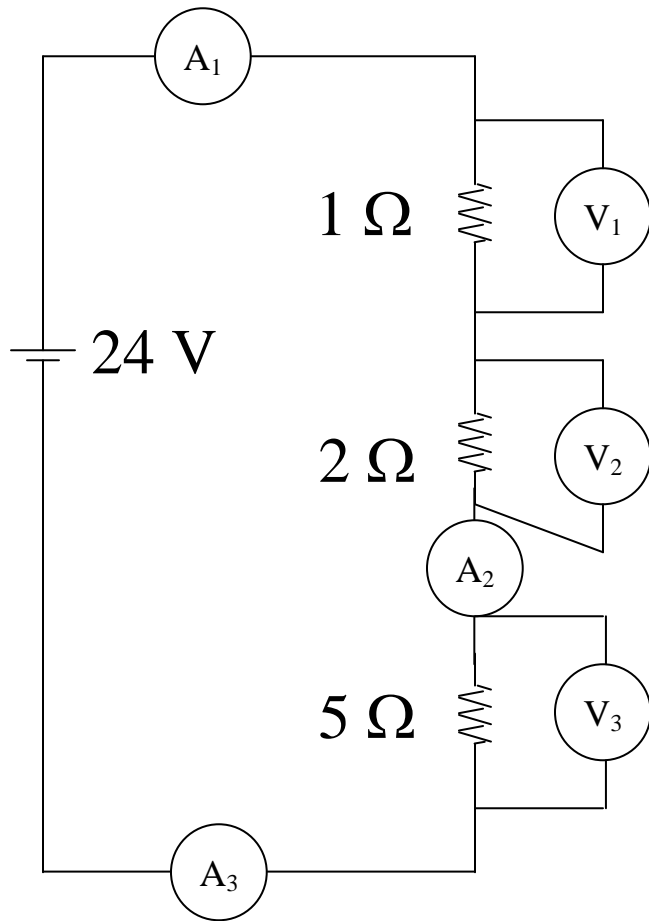

Try these:

(First whiteboard)


What do the meters read? (3 SF)

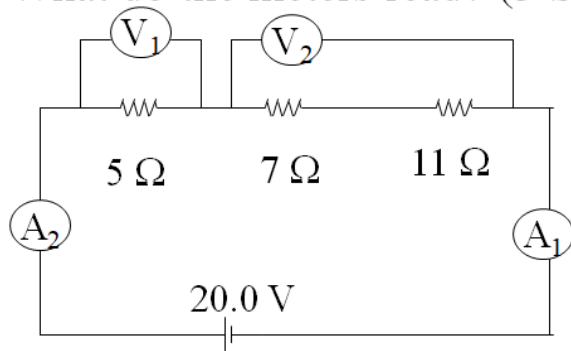


(Both Ammeters: 0.870 A, $V_1 = 4.35\text{ V}$, $V_2 = 15.7\text{ V}$)

(Third Whiteboard)

What do the voltmeters read? (3 SF)

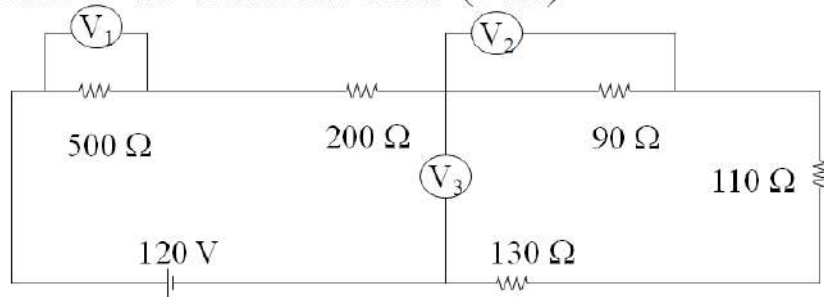


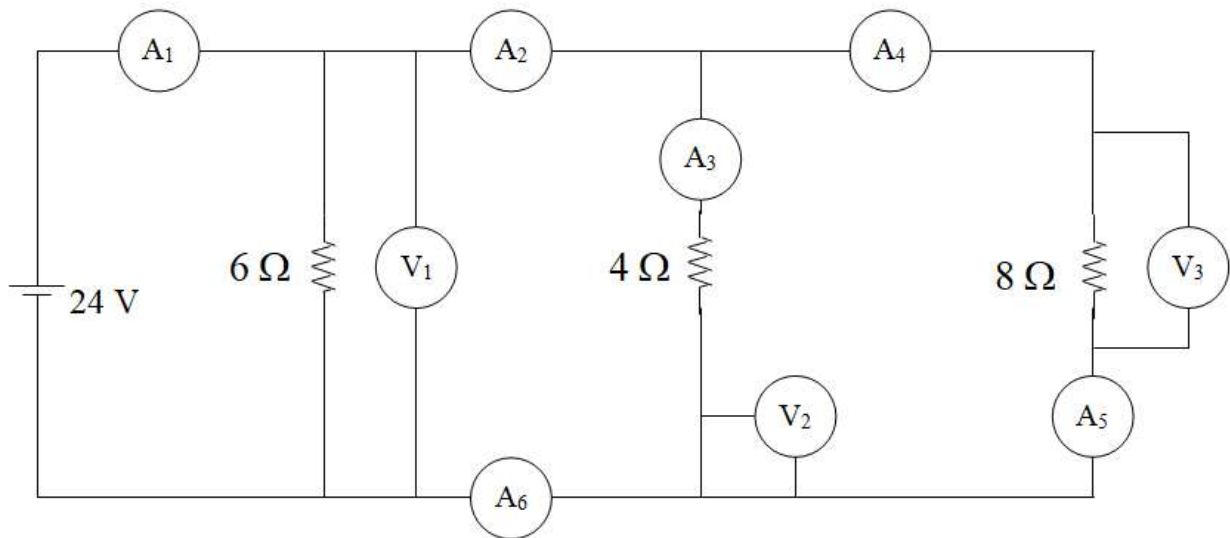($V_1 = 58.3\text{ V}$, $V_2 = 10.5\text{ V}$, $V_3 = 38.4\text{ V}$)



Try These:
(First whiteboard)

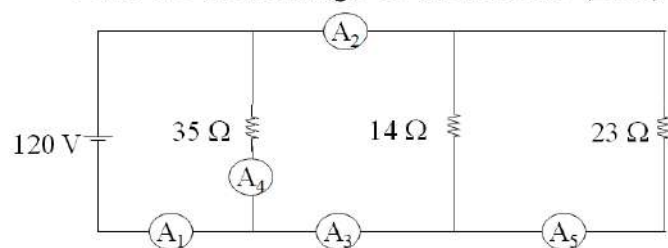
What are the readings on the meters? (2 SF)



($A_1 = 17$, $A_2 = 14$, $A_3 = 14$, $A_4 = 3.4$, $A_5 = 5.2$ A)

(Second whiteboard)

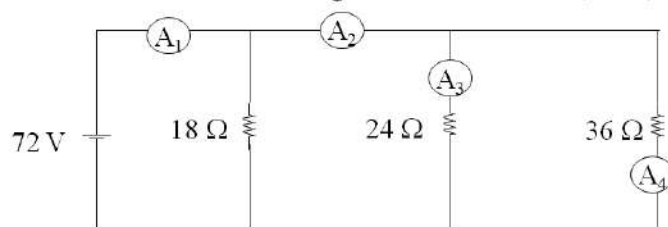What are the readings on the meters? (2 SF)



($A_1 = 9.0$, $A_2 = 5.0$, $A_3 = 3.0$, $A_4 = 2.0$ A)

Noteguide for Series and Parallel Resistance - Videos 18H Name _____


Resistors in Series:

$$R = R_1 + R_2 \dots$$




Resistors in Parallel:
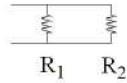
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \dots$$



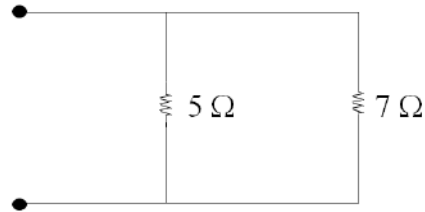Example: What is the resistance from black dot to black dot?



Whiteboards: (Find the resistance from the black dot to the black dot)

1. (177 Ω)

2. (36 Ω)

3. (3.7 Ω)


4. (6 Ω)

5. (8 Ω)

Noteguide for Network Resistance - Videos 18I Name _____


Example 1:

What is the resistance from black dot to black dot?

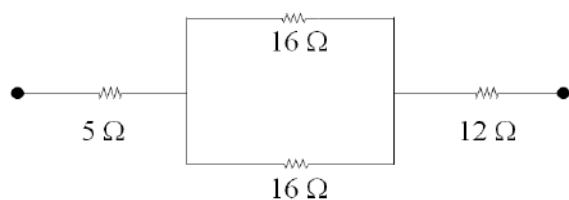


Example 2:

What is the resistance from black dot to black dot? (3 SF)

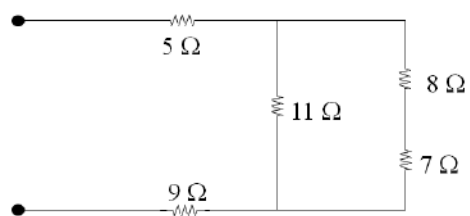



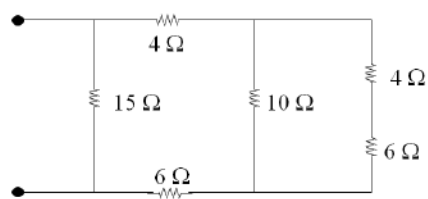
Example 3:

What is the resistance from black dot to black dot? (3 SF)




(Try the whiteboards on the back)

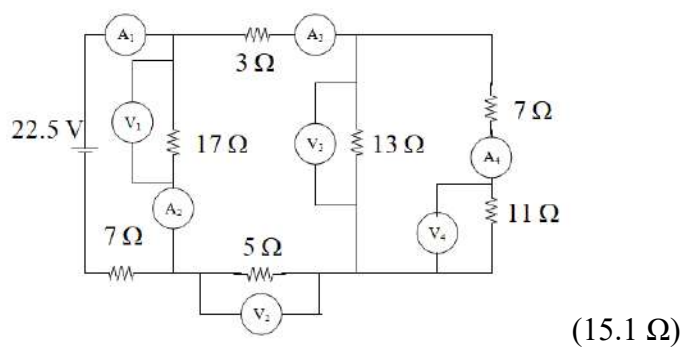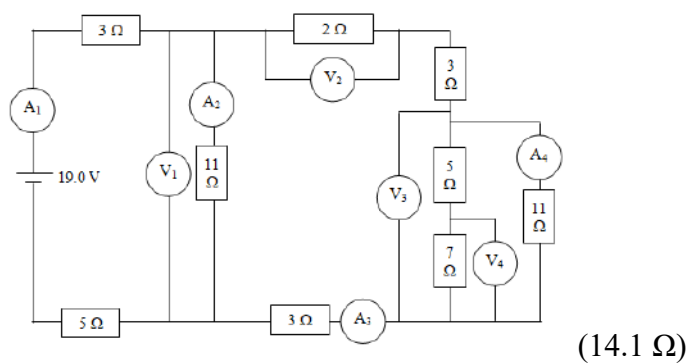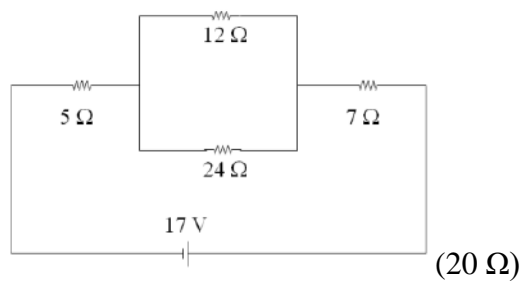Try to find the resistance that is across the battery in each circuit. Ignore the Voltmeters and Ammeters for now:




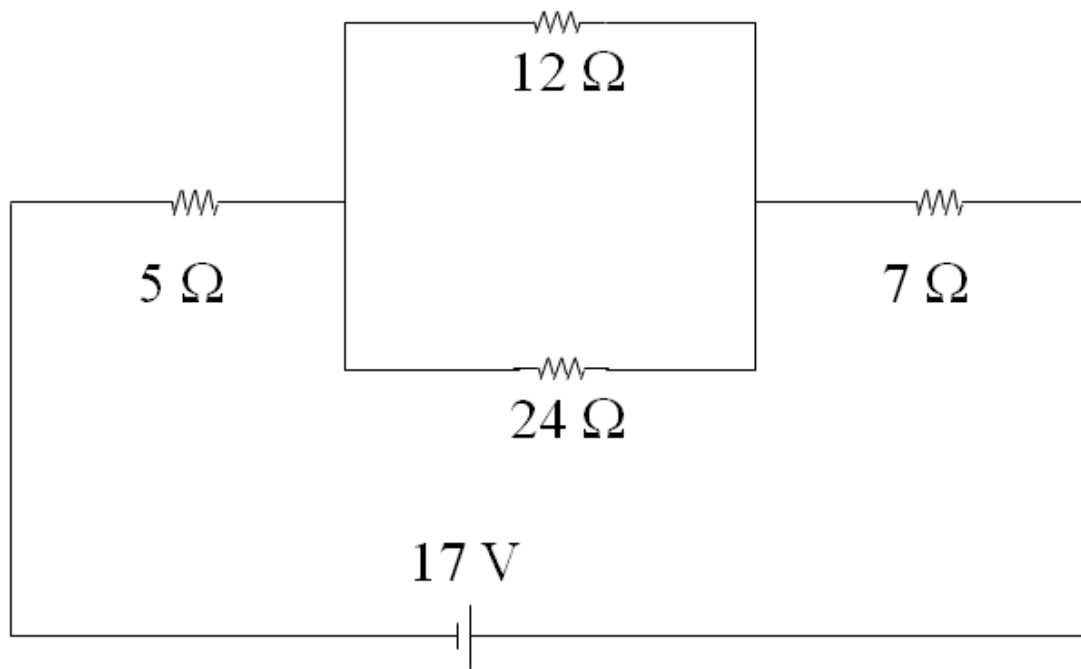Net Example 1 – Find current through and power dissipated by each resistor




R (Ω)	I (A)	P (W)
5	0.85	3.613
12	0.5667	3.853
24	0.2833	1.927
7	0.85	5.058

Net Example 2 (single popper)

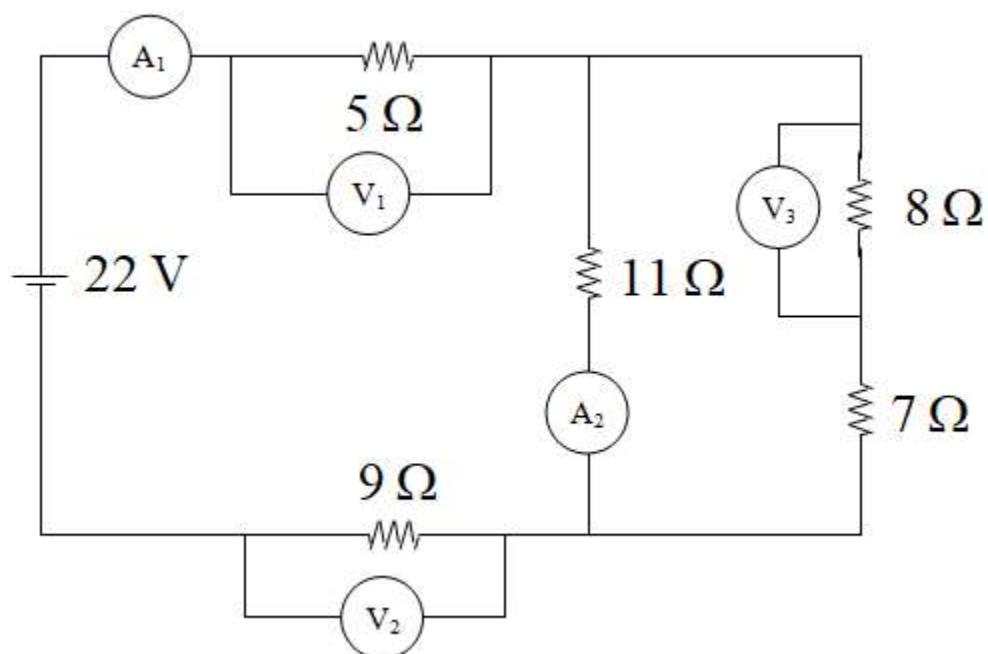


6.3462	
1.0813	A1
5.4064	V1
9.7316	V2
6.862	
0.6238	A2
0.4575	
3.6597	V3

Net Example 3 (double popper)

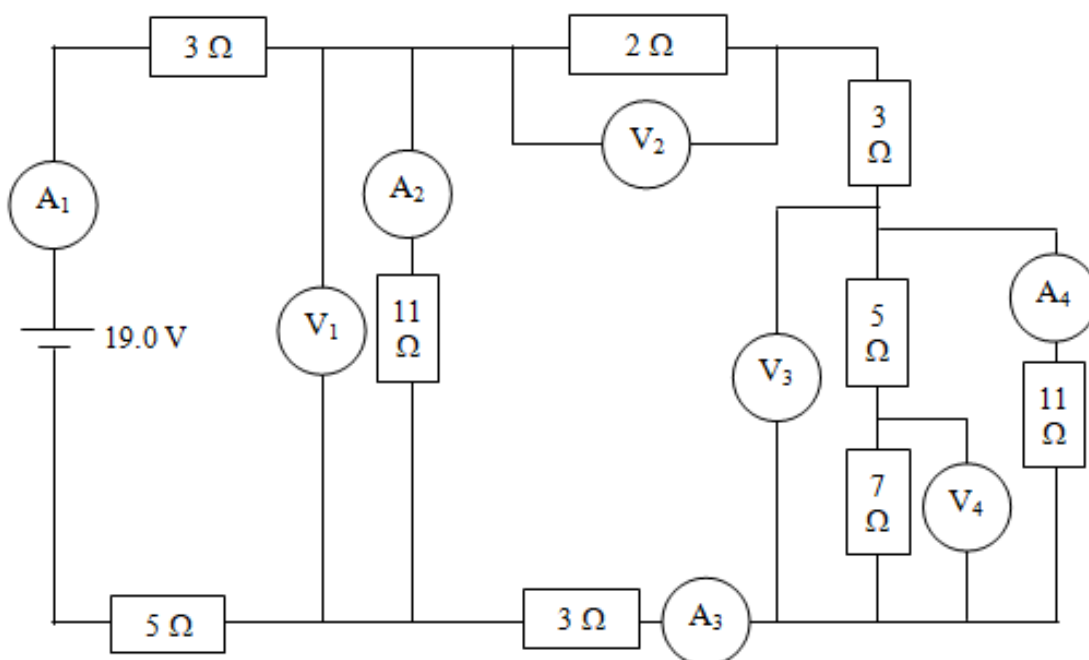

5.73913	
13.73913	
6.108963	
1.346662	A1
8.226707	V1
0.747882	A2
0.598779	A3
1.197559	V2
3.436472	V3
0.312407	A4
0.286373	
2.004609	V4


Net Example 4 (double popper)

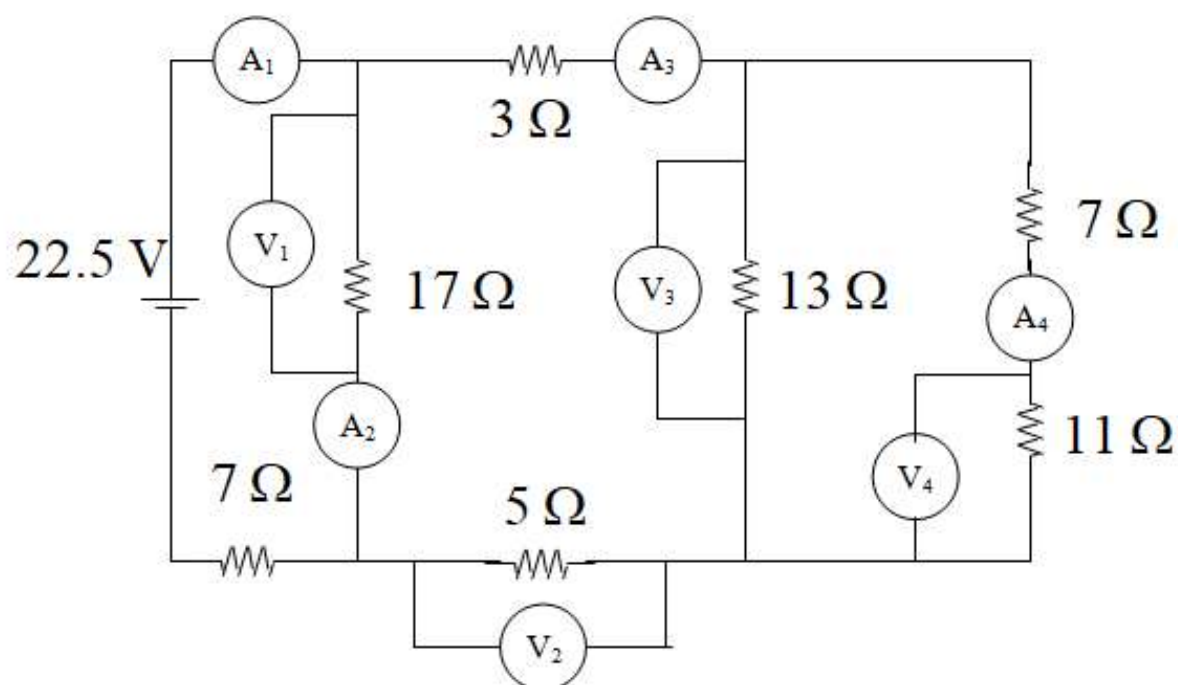

7.548387	
15.54839	
8.120912	
1.488006	A1
12.08396	V1
0.710821	A2
0.777184	A3
3.885921	V2
5.866488	V3
0.325916	A4
3.585076	V4

Junction Rule:

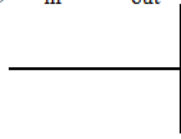
1. For a junction, $\Sigma I_{\text{in}} = \Sigma I_{\text{out}}$ (Junction law = conservation of charge)




Loop Rule

2. For a complete loop, $\Sigma \Delta V = 0$ (Conservation of energy)


For Batteries:

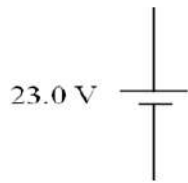


For Resistors:

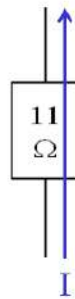

I will give some examples:

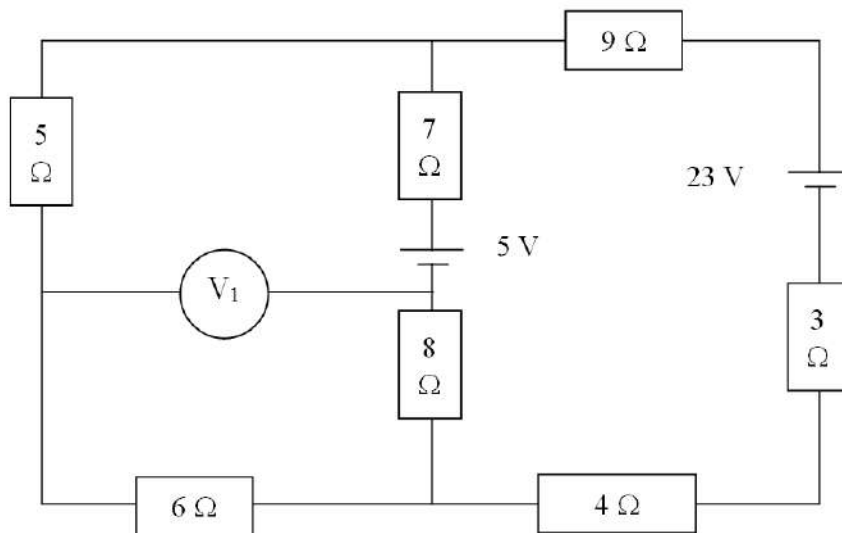

Putting it all together:

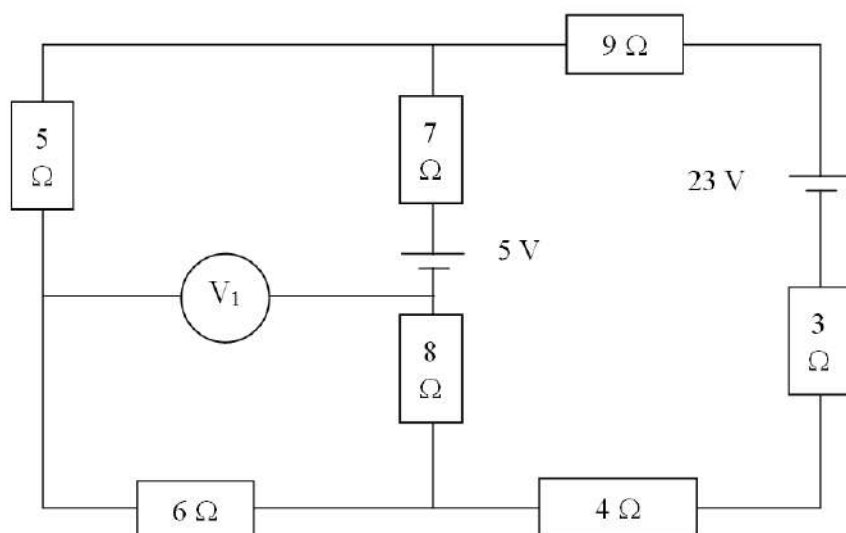

Find Current through:

5 Ω

7 Ω

3 Ω

Voltage across:

8 Ω

9 Ω

Power dissipated by:

4 Ω

6 Ω

|V₁|

5	0.731 A	Down
7	0.203 A	Down
3	0.935 A	Up
8	1.62 V	
9	8.41 V	
4	3.49 W	
6	3.21 W	
V ₁	2.76 V	

