
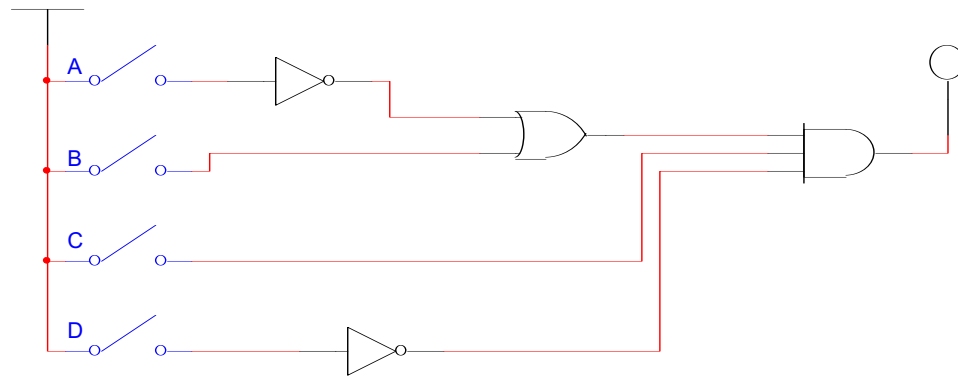


Name _____

NOR NAND QUIZ **practice.doc**

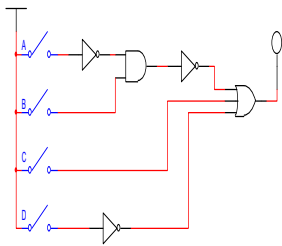

1) Convert the above A-I-O circuit to a **NOR only** circuit, then simplify by crossing out all redundant gates.



2) Convert the above A-I-O circuit to a **NAND only** circuit, then simplify by crossing out all redundant gates.

