

Resistive circuits

- Series
- Parallel
- Series-parallel

Series circuits provide a single path for current flow.

If only one path for current to flow between two points in a circuit, it is a series circuit. The more resistors or load connected in series, the more opposition there is to current flow, the more opposition, the higher the resistance.

Formula: $R_t = R_1 + R_2 + R_3$; *sum of all resistors added together*

Parallel circuits provide two or more paths for current flow.

If more than one path between two points in a circuit with two or more resistors it is a parallel circuit. The more resistors connected in parallel, the less opposition there is to current flow, which equals a lower resistance in a circuit. Total resistance decreases because of additional paths provided. The total resistance is always less than the resistance of any branch.

Formula: $1/R_t = 1/R_1 + 1/R_2 + 1/R_3$; *divide 1 by the resistance (R1, R2, R3...) then add together all values of resistance.*

Series-parallel circuits provides a combination of both types

Current flows through the two branches of parallel portion of the circuit, then the current recombines and flows through the series portions.

Formula: *Use both formulas to compute for answer. Use the parallel formula first then add the series portion to the total resistance from the parallel*