

Electricity



Ohm's Law

- The current of a circuit is directly proportional to the potential difference (voltage) and inversely proportional to the resistance of the circuit
 - $\text{Current} = \text{Voltage} / \text{Resistance}$



Ohm's Law

- Variables:

- Current: I
- Potential Difference (Voltage): V
- Resistance: R

- Units:

- Current: Amps (A)
- Potential Difference: Volts (V)
- Resistance: Ohms (Ω)

- Formula: $V = IR$

$$V = IR$$

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$



Ohm's Law

I

1. How much current flows through a circuit with a 12Ω resistor connected to two 1.5V batteries?

$$V = 3V$$

$$I = \frac{V}{R} = \frac{3V}{12\Omega} = 0.25A$$



Ohm's Law

2. What is the ^Rresistance^V of a circuit with 120V of potential difference and 60A of current^I?

$$R = \frac{V}{I} = \frac{120V}{60A} = 2\Omega$$



Ohm's Law


3. What is the potential difference of a circuit with two 30Ω resistors and $3A$ of current?

$$R = 60\Omega \quad I$$

$$V = IR = (3A)(60\Omega) = 180V$$



Electricity & Power

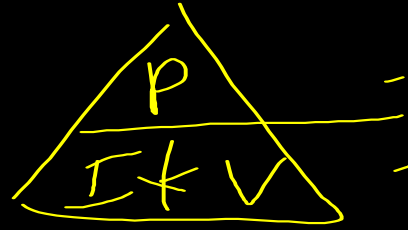

- Electrical power is the rate at which another form of energy is converted into electrical energy
 - Unit: Watt ($1\text{W}=1\text{J/s}$)
 - $P \text{ (watts)} = I \text{ (amps)} \times V \text{ (volts)}$
- Electrical energy is calculated by multiplying power by time
 - Unit: Kilowatt-hour (kW-h)
 - $E \text{ (kilowatt-hours)} = P \text{ (kilowatts)} \times t \text{ (hours)}$



Electrical Power

1. How much ^Ppower is contained in a circuit with 0.43A of current connected to a 9V battery?

$$P = IV = (0.43\text{ A})(9\text{ V}) =$$

$$3.9\text{ W}$$



Electrical Power



2. What is the current in a lamp connected to a 120V outlet with a 60W bulb?

$$I = \frac{P}{V} = \frac{60W}{120V} = 0.5A$$



Electrical Power



3. What is the voltage of a circuit with 15W of power and a current of 8A? I P

$$V = \frac{P}{I} = \frac{15W}{8A} = 1.9V$$

